

Instruction: This is an in class assignment.

Member:

1. Name: _____ Code: _____

2. Name: _____ Code: _____

1. The waveform for the current in a $200\text{-}\mu\text{F}$ capacitor is shown in Fig ?? . Determine the waveform for the capacitor voltage.

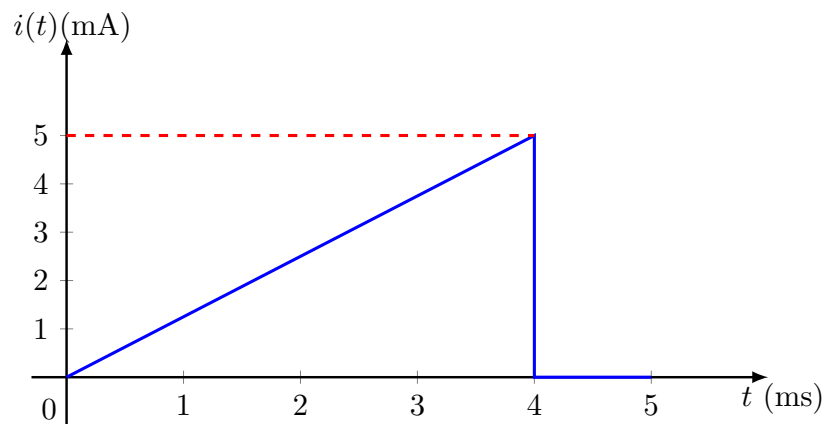


Figure 1: For Question 1

Solution: We have

$$v_C(t) = \frac{1}{C} \int_{t_0}^t i_C(\tau) d\tau + v_C(t_0)$$

From the Fig ??, we have

$$i_C(t) = \begin{cases} 0 \text{ A}, & t < 0 \text{ ms} \\ \frac{5}{4}t \text{ A}, & 0 \leq t < 4 \text{ ms} \\ 0 \text{ A}, & t \geq 4 \text{ ms} \end{cases}, \quad v_C(t) = \begin{cases} 0 \text{ V}, & t < 0 \text{ ms} \\ 3.125 \times 10^3 t^2 \text{ V}, & 0 \leq t < 4 \text{ ms} \\ 0.05 \text{ V}, & t \geq 4 \text{ ms} \end{cases}$$

Note: $v_C(t = 4\text{ms}) = 3.125 \times 10^3 (4 \times 10^{-3})^2 = 0.05 \text{ V}$. The $v_C(t > 4\text{ms}) = \frac{1}{C} \int_{4 \times 10^{-3}}^{\infty} 0 d\tau + v_C(4 \times 10^{-3}) = 0.05 \text{ V}$. The plot of $v_C(t)$ is shown in Fig ??.

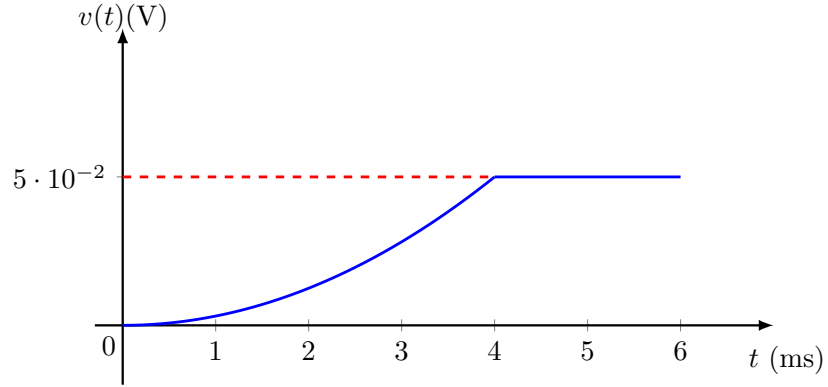


Figure S1: $v_C(t)$

2. The current in a 10-mH inductor has the waveform shown in Fig. ???. Determine the voltage waveform.

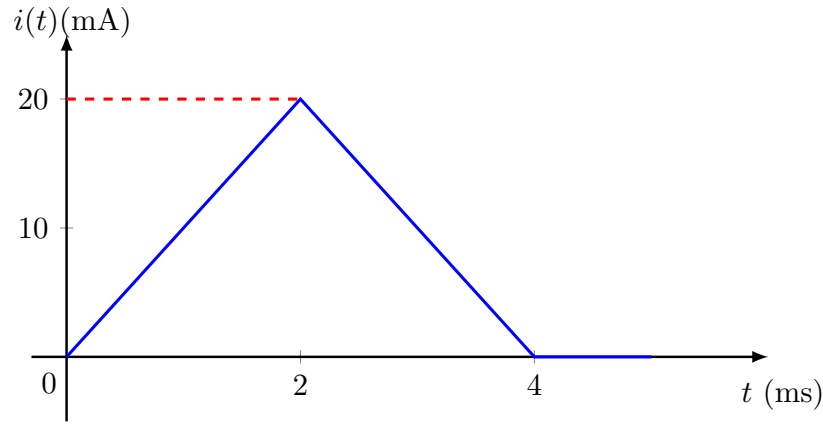


Figure 2: For Question 2

Solution: The equation for the current waveform in the specified time intervals are

$$i(t) = \begin{cases} 0 \text{ A}, & t < 0 \\ 10t \text{ A}, & 0 \leq t \leq 2 \text{ ms} \\ -10t + 40 \times 10^{-3} \text{ A}, & 2 \text{ ms} \leq t \leq 4 \text{ ms} \\ 0 \text{ A}, & t \geq 4 \text{ ms} \end{cases}$$

From $v(t) = L di(t)/dt$, we have

$$v(t) = \begin{cases} 0 \text{ mV}, & t < 0 \\ 100 \text{ mV}, & 0 \leq t \leq 2 \text{ ms} \\ -100 \text{ mV}, & 2 \text{ ms} \leq t \leq 4 \text{ ms} \\ 0 \text{ mV}, & t \geq 4 \text{ ms} \end{cases}$$

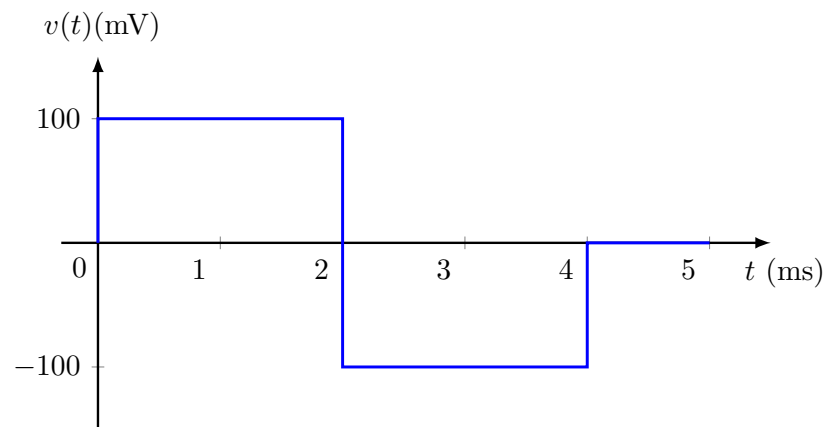


Figure S2: Voltage $v(t)$

Then the voltage waveform is shown in Fig ??

□