

# INC 122 : RLC Circuits

---

Dr.-Ing. Sudchai Boonto  
Assistant Professor

Department of Control System and Instrumentation Engineering  
King Mongkut's Unniversity of Technology Thonburi Thailand

February 25, 2025


# Learning Outcomes

Students should be able to:

- ▶ Determine the voltages and currents in the second-order transient circuits.
- ▶ Use Graphical and Symbolic tools to plot and check the calculation results.

# Parallel RLC Circuit

Basic parallel RLC circuits

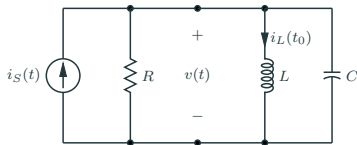

Using KCL, we have


$$\frac{v(t)}{R} + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i_L(t_0) + C \frac{dv}{dt} = i_S(t)$$

Derivative with respect to  $t$  of both sides, we obtain

$$C \frac{d^2 v}{dt^2} + \frac{1}{R} \frac{dv}{dt} + \frac{v(t)}{L} = \frac{di_S}{dt}$$

# Series RLC Circuit

Basic series RLC circuits

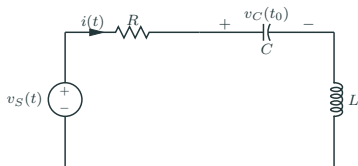

Using KVL, we have

$$Ri(t) + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v_C(t_0) + L \frac{di}{dt} = v_S(t)$$

Derivative with respect to  $t$  of both sides, we obtain

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i(t)}{C} = \frac{dv_S}{dt}$$

Both series and parallel circuits lead to a second-order differential equation with constant coefficients.

# General Form of 2nd Order Circuit Equation

The RLC circuits, both parallel and series, have the same form equations:

$$\frac{d^2x(t)}{dt^2} + a_1 \frac{dx(t)}{dt} + a_0x(t) = f(t)$$

If  $x(t) = x_p(t)$ , it is a solution of the general equation, and if  $x(t) = x_c(t)$ , it is a solution to the homogeneous equation

$$\frac{d^2x(t)}{dt^2} + a_1 \frac{dx(t)}{dt} + a_0x(t) = 0$$

Then

$$x(t) = x_p(t) + x_c(t)$$

is the solution of the general equation.

# General Form of 2nd Order Circuit Equation

Using the fact that DC sources, i.e.,  $f(t) = A$  will reach all voltages and currents of the element is constant, i.e.,  $x_p(t) = \text{constant}$ . Then, by substituting this result back to the equation,

$$\frac{d^2 x_p(t)}{dt^2} + a_1 \frac{dx_p(t)}{dt} + a_2 x_p(t) = A$$

$$a_0 x_p(t) = A$$

$$x_p(t) = \frac{A}{a_0}$$

$$x(t) = \frac{A}{a_0} + x_c(t)$$

The next step is to find the solution  $x_c(t)$  to the homogeneous equation. Rewrite the equation in the form

$$\frac{d^2 x_c(t)}{dt^2} + 2\zeta\omega_n \frac{dx_c(t)}{dt} + \omega_n^2 x_c(t) = 0,$$

where  $a_1 = 2\zeta\omega_n$  and  $a_0 = \omega_n^2$ .

# General Form of 2nd Order Circuit Equation

To satisfy the homogenous equation, the first and second-order derivatives of  $x_c(t)$  must have the same form, hence

$$x_c(t) = Ke^{\lambda t}$$

and

$$\lambda^2 Ke^{\lambda t} + 2\zeta\omega_n \lambda Ke^{\lambda t} + \omega_n^2 Ke^{\lambda t} = 0$$

$$\lambda^2 + 2\zeta\omega_n \lambda + \omega_n^2 = 0 \text{ ( note } Ke^{\lambda t} \neq 0 \forall t)$$

We call

- ▶  $\lambda^2 + 2\zeta\omega_n \lambda + \omega_n^2 = 0$  is called **characteristic equation**.
- ▶  $\zeta$  is called the **damping ratio**.
- ▶  $\omega_n$  is referred to as the **undamped natural frequency**.

# General Form of 2nd Order Circuit Equation

$$\lambda^2 + 2\zeta\omega_n\lambda + \omega_n^2 = 0$$

$$\lambda = \frac{-2\zeta\omega_n \pm \sqrt{4\zeta^2\omega_n^2 - 4\omega_n^2}}{2}$$

$$= -\zeta\omega_n \pm \omega_n\sqrt{\zeta^2 - 1}$$

$$\lambda_1 = -\zeta\omega_n + \omega_n\sqrt{\zeta^2 - 1}, \quad \lambda_2 = -\zeta\omega_n - \omega_n\sqrt{\zeta^2 - 1}$$

Both  $\lambda_i$  are the solution of the characteristic equation, then the complementary solution of the general form differential equation is of the form

$$x_c(t) = K_1e^{\lambda_1 t} + K_2e^{\lambda_2 t},$$

and

$$x_c(0) = K_1 + K_2, \quad \left. \frac{dx_c}{dt} \right|_{t=0} = \lambda_1 K_1 + \lambda_2 K_2$$

$x_c(t)$  is an unforced response of the network (no input). There are three possible cases.




# The Overdamped Circuit

**Case 1**  $\zeta > 1$  The term  $\sqrt{\zeta^2 - 1}$  is greater than 0. The natural frequencies  $\lambda_1$  and  $\lambda_2$  are real and unequal. We have

$$x_c(t) = K_1 e^{\lambda_1 t} + K_2 e^{\lambda_2 t}$$

This case is called **overdamped response**.

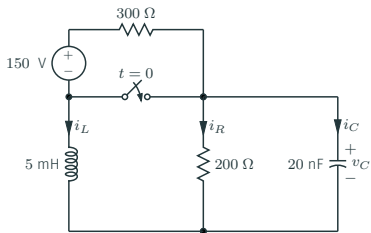**Example:** Find an expression for  $v_C(t)$  valid for  $t > 0$ .




At  $t < 0$  :

$$v_C(0^-) = 150 \frac{200}{300 + 200} = 60 \text{ V}$$

$$i_L(0^-) = -\frac{150}{500} = -0.3 \text{ A}$$

# The Overdamped Circuit

At  $t > 0$ , using KCL:

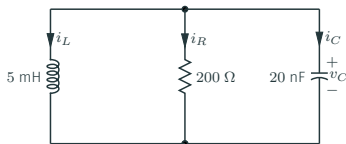

$$i_L + i_R + C \frac{dv_C}{dt} = 0$$

$$\frac{1}{L} \int_{t_0}^t v_C(\tau) d\tau + \frac{v_C}{R} + C \frac{dv_C}{dt} = 0$$

$$\frac{d^2 v_C}{dt^2} + \frac{1}{RC} \frac{dv_C}{dt} + \frac{1}{LC} v_C(t) = 0$$

We have

$$2\zeta\omega_n = \frac{1}{RC} = 2.5 \times 10^5, \quad \omega_n = \sqrt{\frac{1}{LC}} = 1 \times 10^5 \text{ rad/s}$$

$$2\zeta\omega_n = 2.5 \times 10^5, \quad \Rightarrow \quad \zeta = 1.25$$

$$\begin{aligned} \lambda_{1,2} &= -\zeta\omega_n \pm \omega_n \sqrt{\zeta^2 - 1} = 1.25 \times 10^5 \pm 1 \times 10^5 \sqrt{1.25^2 - 1} \\ &= -5 \times 10^4, -2 \times 10^5 \end{aligned}$$

Then  $v_C(t) = K_1 e^{-50000t} + K_2 e^{-200000t}$  V.

# The Overdamped Circuit

We have

$$v_C(0^-) = 60 = K_1 + K_2$$

From

$$\begin{aligned} i_L + i_R + C \frac{dv_C}{dt} &= 0 \\ \left. \frac{dv_C}{dt} \right|_{t=0^-} &= \dot{v}_C(0^-) = -\frac{i_L(0^-)}{C} - \frac{v_C(0^-)}{RC} \\ &= -\frac{-0.3}{20 \text{ nF}} - \frac{60}{200 \times 20 \text{ nF}} = 0 \\ &= -50000K_1 - 200000K_2 \end{aligned}$$


We have  $K_1 = 80$  and  $K_2 = -20$ . So we obtain

$$v_C(t) = 80e^{-50000t} - 20e^{-200000t} \text{ V}$$


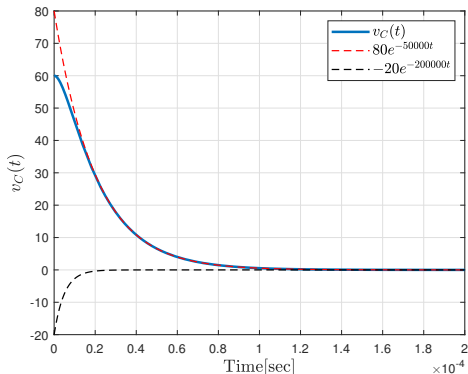
# The Overdamped Circuit

```
1 syms vc(t) t
2 R = 200; L = 5e-3; C = 20e-9;
3 eqn = diff(vc,t,2) + (1/(R*C))*diff(vc,t)
      + (1/(L*C))*vc(t) == 0;
4 Dvc = diff(vc,t);
5
6 cond1 = vc(0) == 60; cond2 = Dvc(0) == 0;
7 conds = [cond1; cond2];
8 vc = dsolve(eqn, conds);

8 yout = fplot(vc, [0, 2e-4], 'linewidth', 2)
      ;
9 tt = yout.XData;
10 y1 = 80*exp(-5e4*tt);
11 y2 = -20*exp(-2e5*tt);
12 hold on
13 plot(tt, y1, 'r--', tt, y2, 'k--', '
      linewidth', 1)
14 grid on ; hold off
```



# The Overdamped Circuit

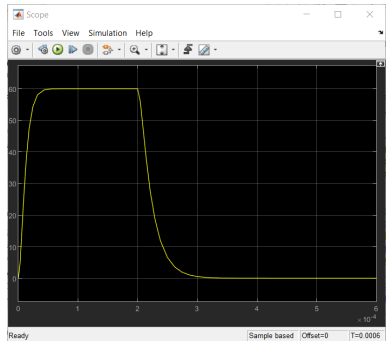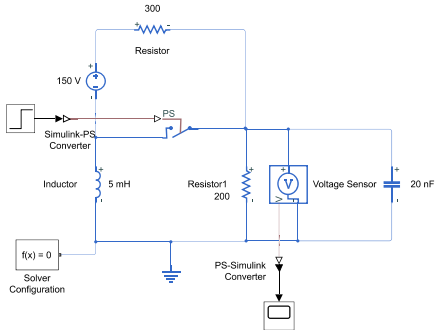

In Simscape the switch is closed at  $t = 2 \times 10^{-4}$  sec.

# The underdamped Circuit

**Case 2**  $\zeta < 1$  The term  $\sqrt{\zeta^2 - 1}$  is less than 0. The roots of the characteristic equation can be written as

$$\begin{aligned}\lambda &= -\zeta\omega_n \pm \omega_n \sqrt{\zeta^2 - 1} \quad \zeta^2 - 1 \text{ is negative} \\ &= -\zeta\omega_n \pm \omega_n \sqrt{(-1)(1 - \zeta^2)} = -\zeta\omega_n \pm j\omega_n \sqrt{1 - \zeta^2} = -\sigma \pm j\omega\end{aligned}$$

This case is called **underdamped response**. We have


$$x_c(t) = Ce^{-\sigma t} \cos(\omega t + \theta), \quad \sigma = \zeta\omega_n \text{ and } \omega = \omega_n \sqrt{1 - \zeta^2}$$

## complex conjugate roots

$$\begin{aligned}x_c(t) &= K_1 e^{(-\sigma + j\omega)t} + K_2 e^{(-\sigma - j\omega)t} \\ K_1 &= \frac{C}{2} e^{j\theta}, \quad K_2 = \frac{C}{2} e^{-j\theta} \\ x_c(t) &= \frac{C}{2} e^{-\sigma t} \left( e^{j(\omega t + \theta)} + e^{-j(\omega t + \theta)} \right) \\ &= C e^{-\sigma t} \cos(\omega t + \theta) \quad \text{using Euler's identity}\end{aligned}$$

# The underdamped Circuit

Determine  $i_L(t)$  for the circuit.

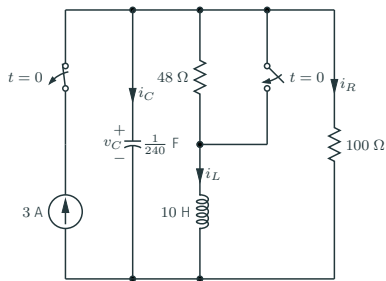


At  $t > 0$ , the circuit is changed to  $\Rightarrow$

At  $t < 0$ , capacitor acts as an open circuit, and inductor acts as a short circuit.

$$i_L(0^-) = 3 \left( \frac{100}{100 + 48} \right) = 2.027 \text{ A}$$
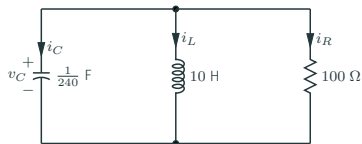
$$v_C(0^-) = 48i_L(0^-) = 97.30 \text{ V}$$



# The underdamped Circuit

Using KCL, we have

$$\begin{aligned}i_C + i_L + i_R &= 0 \\C \frac{dv_C}{dt} + \frac{1}{L} \int_{-\infty}^t v_C(\tau) d\tau + \frac{v_C}{R} &= 0 \\ \frac{d^2 v_C}{dt^2} + \frac{1}{RC} \frac{dv_C}{dt} + \frac{1}{LC} v_C(t) &= 0\end{aligned}$$

Substituting all values, we have

$$\frac{d^2 v_C}{dt^2} + 2.4 \frac{dv_C}{dt} + 24 v_C(t) = 0,$$

where

$$\omega_n = \sqrt{24} = 4.899 \text{ rad/sec}, \quad 2\zeta\omega_n = 2.4 \Rightarrow \zeta = 0.245$$

$$\lambda = -\zeta\omega_n \pm j\omega_n\sqrt{1-\zeta^2} = -1.2 \pm j4.75$$



# The underdamped Circuit

$$\begin{aligned}v_C(t) &= K e^{-1.2t} \cos(4.75t + \theta) \\v_C(0^-) &= 97.30 = K \cos(\theta)\end{aligned}$$

Since  $i_C + i_L + i_R = 0$ , we have

$$\left. \frac{dv_C}{dt} \right|_{t=0^-} = -\frac{i_L(0^-)}{C} - \frac{v_C(0^-)}{RC} = -486.48 - 233.5200 = -720$$

Then,

$$\left. \frac{dv_C}{dt} \right|_{t=0^-} = \dot{v}_C(0^-) = -720 = -1.2K \cos(\theta) - 4.75K \sin(\theta)$$

$$K \sin(\theta) = (-720 + 1.2(97.3))/(-4.75) = 127$$

$$K = \sqrt{97.3^2 + 127^2} = 160$$

$$\theta = \tan^{-1} \frac{127}{97.30} = 52.54^\circ$$


$$v_C(t) = 160e^{-1.2t} \cos(4.75t + 52.54^\circ)$$

# The underdamped Circuit

Note that,

$$\begin{aligned}i_L(t) &= -\frac{1}{240} \frac{dv_C}{dt} - \frac{v_C}{100} \\&= -\frac{1}{240} (-192e^{-1.2t} \cos(4.75t + 52.54^\circ) - 760e^{-1.2t} \sin(4.75t + 52.54^\circ)) \\&\quad - 1.6e^{-1.2t} \cos(4.75t + 52.54^\circ) \\&= -0.8e^{-1.2t} \cos(4.75t + 52.54^\circ) + 3.167e^{-1.2t} \sin(4.75t + 52.54^\circ) \\&= -0.8e^{-1.2t} (\cos(4.75t) \cos(52.54^\circ) - \sin(4.75t) \sin(52.54^\circ)) \\&\quad + 3.167e^{-1.2t} (\sin(4.75t) \cos(52.54^\circ) + \sin(52.54^\circ) \cos(4.75t)) \\&= e^{-1.2t} (-0.4866 \cos(4.75t) + 0.6350 \sin(4.75t)) \\&\quad + e^{-1.2t} (1.9262 \sin(4.7t) + 2.5139 \cos(4.75t)) \\&= e^{-1.2t} (2.0273 \cos(4.75t) + 2.5612 \sin(4.75t)) \\&= 3.266e^{-1.2t} \cos(4.75t - 51.34^\circ)\end{aligned}$$

# The underdamped Circuit

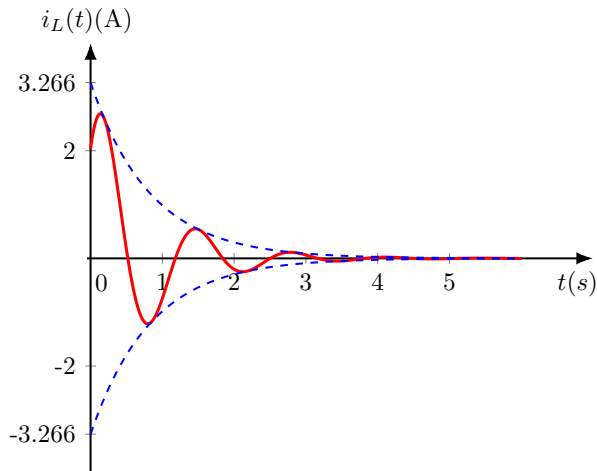

# The critically damped Circuit

**Case 3**  $\zeta = 1$  The term  $\sqrt{\zeta^2 - 1}$  is 0. The roots of the characteristic equation are repeated as

$$\lambda_1 = \lambda_2 = -\zeta\omega_n$$

This case is called **critically damped** response. We have

$$x_c(t) = B_1 e^{\lambda_1 t} + B_2 t e^{\lambda_2 t}.$$

## Proof\*

Consider the following case

$$\frac{d^2 x(t)}{dt^2} + 2\alpha \frac{dx(t)}{dt} + \alpha^2 x(t) = 0$$

Since the roots are equal to  $\alpha$ , the homogenous solution could be (wrong!)

$$x_c(t) = K_1 e^{-\alpha t} + K_2 e^{-\alpha t} = K_3 e^{-\alpha t}$$

# The critically damped Circuit

## Proof\*

One know solution is

$$x_{c1}(t) = K_3 e^{-\alpha t} \quad \text{and} \quad x_{c2}(t) = x_{c1}(t)v(t) = K_3 e^{-\alpha t} v(t)$$

The equation becomes

$$\frac{d^2}{dt^2} [K_3 e^{-\alpha t} v(t)] + 2\alpha \frac{d}{dt} [K_3 e^{-\alpha t} v(t)] + \alpha^2 K_3 e^{-\alpha t} v(t) = 0$$

Evaluating the derivatives, we obtain

$$\begin{aligned} \frac{d}{dt} [K_3 e^{-\alpha t} v(t)] &= -K_3 \alpha e^{-\alpha t} v(t) + K_3 e^{-\alpha t} \frac{dv(t)}{dt} \\ \frac{d^2}{dt^2} [K_3 e^{-\alpha t} v(t)] &= K_3 \alpha^2 e^{-\alpha t} v(t) - 2K_3 \alpha e^{-\alpha t} \frac{dv(t)}{dt} + K_3 e^{-\alpha t} \frac{d^2 v(t)}{dt^2} \end{aligned}$$

# The critically damped Circuit

## Proof\*

Substituting these expressions into the preceding equation yields

$$K_3 e^{-\alpha t} \frac{d^2 v(t)}{dt^2} = 0$$

Therefore,


$$\frac{d^2 v(t)}{dt^2} = 0 \Rightarrow v(t) = A_1 + A_2 t$$

Therefore, the general solution is

$$x_{c2}(t) = x_{c1}(t)v(t) = K_3 e^{-\alpha t} [A_1 + A_2 t] = B_1 e^{\lambda t} + B_2 t e^{\lambda t}$$
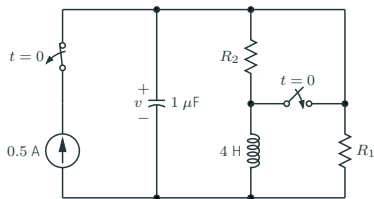
# The critically damped Circuit

Select a value for  $R_1$  such that the circuit in Fig. below will be characterized by a critically damped response for  $t > 0$ , and a value for  $R_2$  such that  $v(0^-) = 100$  V. Find  $v(t)$  at  $t = 1$  ms.




At  $t > 0$ , the circuit is changed to  $\Rightarrow$

At  $t < 0$ , capacitor acts as an open circuit, and inductor acts as a short circuit.

$$i_L(0^-) = 0.5 \left( \frac{R_1}{R_1 + R_2} \right) \text{ A}$$
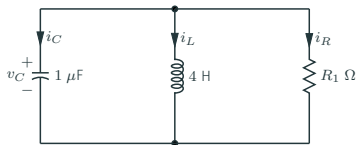
$$v(0^-) = 0.5 \left( \frac{R_1 R_2}{R_1 + R_2} \right) \text{ V}$$



# The critically damped Circuit

Using KCL, we have

$$i_C + i_L + i_R = 0$$
$$\frac{d^2 v_C}{dt^2} + \frac{1}{R_1 C} \frac{dv_C}{dt} + \frac{1}{LC} v_C(t) = 0$$

To have a critically damped response, we have to have ( $\lambda^2 + 2\zeta\omega_n\lambda + \omega_n^2 = 0, \zeta = 1$ )

$$\frac{1}{2R_1 C} = \sqrt{\frac{1}{LC}} = 500$$
$$R_1 = \frac{1}{10 \times 10^3 (1 \times 10^{-6})} = 1000 \, \Omega$$

We need  $v(0^-) = 100 \, \text{V}$ , so

$$v(0^-) = 0.5 \left( \frac{R_1 R_2}{R_1 + R_2} \right) = 100 \quad \Rightarrow \quad R_2 = 250 \, \Omega$$

$$i_L(0^-) = 0.4 \, \text{A}$$



# The critically damped Circuit

Note we have  $\lambda = \frac{-1}{2R_1C} = -500$ , then

$$v(t) = B_1e^{-500t} + B_2te^{-500t}$$
$$v(0^-) = 100 = B_1$$

From  $i_C + i_L + i_R = 0$ , we have

$$\left. \frac{dv}{dt} \right|_{t=0^-} = \dot{v}_C(0^-) = \frac{i_L(0^-)}{C} - \frac{v_C(0^-)}{R_1C} = -5 \times 10^5 \text{ V/s}$$

From 
$$\frac{dv}{dt} = -5 \times 10^4 e^{-500t} + B_2 e^{-500t} - 500 B_2 t e^{-500t}$$

$$\left. \frac{dv}{dt} \right|_{t=0^-} = \dot{v}_C(0^-) = -5 \times 10^5 = -5 \times 10^4 + B_2$$


$$B_2 = -4.5 \times 10^5$$

Then

$$v(t) = 100e^{-500t} - 4.5 \times 10^5 te^{-500t} \text{ and } v(t = 1 \times 10^{-3}) = -212.2856 \text{ V.}$$
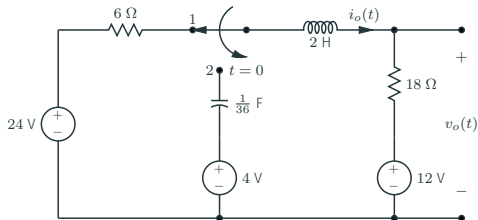
# RLC Circuit: Hard Example

The switch in the network in Fig. below moves from position 1 to position 2 at  $t = 0$ . Compute  $i_o(t)$  for  $t > 0$  and use this current to determine  $v_o(t)$  for  $t > 0$ .




At  $t < 0$ , we have

$$i_L(0^-) = i_o(0^-) = \frac{24 - 12}{24} = 0.5 \text{ A}$$

$$v_C(0^-) = 0 \text{ V}$$

$$v_o(0^-) = 0.5(18) = 9 + 12 = 21 \text{ V}$$

At  $t > 0$

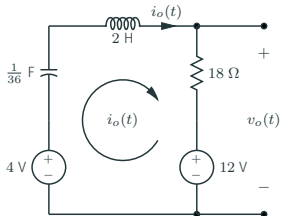

Using KVL, we have

$$-4 + 36 \int_{-\infty}^t i_o(\tau) d\tau + 2 \frac{di_o}{dt} + 18i_o(t) + 12 = 0$$

$$\frac{d^2 i_o}{dt^2} + 9 \frac{di_o}{dt} + 18i_o(t) = 0$$

## RLC Circuit: Hard Example

At the steady-state, the capacitor acts as an open circuit. Then  $i_{op}(t)$  (particular solution) is zero, and  $i_{op}(t) = 0$ . Considering the transient response, we obtain

$$\frac{d^2 i_o}{dt^2} + 9 \frac{di_o}{dt} + 18 i_o(t) = 0$$
$$\lambda_{1,2} = -\frac{9}{2} \pm \frac{\sqrt{81 - 72}}{2} = -\frac{9}{2} \pm \frac{3}{2} = -3, -6$$

We have a complementary solution

$$i_{oc}(t) = K_1 e^{-3t} + K_2 e^{-6t} \quad \Rightarrow \quad i_{oc}(0^-) = 0.5 = K_1 + K_2$$


Since  $\left. \frac{di_o}{dt} \right|_{t=0^-} = -9i_o(0^-) - \frac{v_C(0^-)}{2} - 4 = -\frac{17}{2}$ , then

$$-\frac{17}{2} = -3K_1 - 6K_2 \quad \Rightarrow \quad K_1 = -\frac{11}{6}, \quad K_2 = \frac{14}{6}$$


$$i_{oc}(t) = i_o(t) = -\frac{11}{6} e^{-3t} + \frac{14}{6} e^{-6t} \text{ A}$$

$$v_o(t) = 12 + 18i_o(t) = 12 - 33e^{-3t} + 42e^{-6t} \text{ V}$$
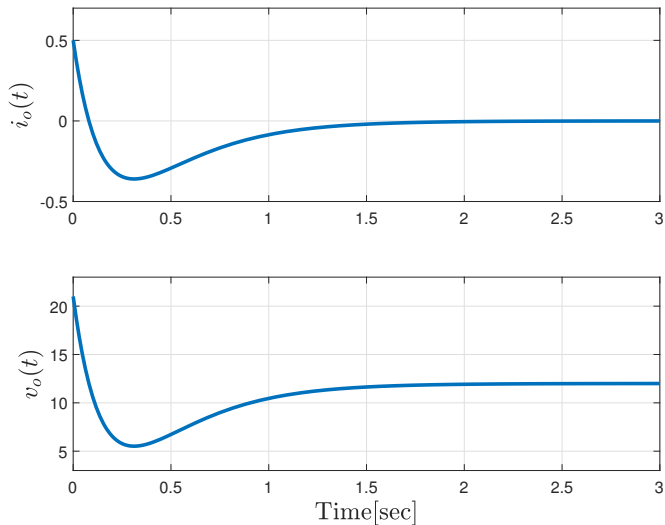
## RLC Circuit: Hard Example (Matlab Plot)



# RLC Circuit: Hard Example II

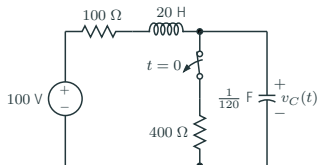


At  $t = 0^-$ , we have

$$i_L(0^-) = \frac{100}{100 + 400} = 0.2 \text{ A}, \quad v_C(0^-) = \frac{100(400)}{100 + 400} = 80 \text{ V}$$

Find  $v_C(t)$  at time  $t > 0$ .

The circuit at time  $t > 0$ .

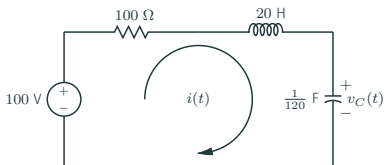

$$Ri(t) + L \frac{di}{dt} + v_C(t) = 100, \quad i_C(t) = C \frac{dv_C}{dt}$$

$$\frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{1}{LC} v_C(t) = \frac{100}{LC}$$

$$\frac{d^2 v_C}{dt^2} + 5 \frac{dv_C}{dt} + 6 v_C(t) = 600$$

## RLC Circuit: Hard Example II

The particular solution is

$$6v_{Cp}(t) = 600 \implies v_{Cp}(t) = 100 \text{ V}$$

The characteristic solution is

$$\lambda^2 + 5\lambda + 6 = 0 \implies \lambda_{1,2} = -2, -3$$

Then the complementary solution is

$$v_{Cc}(t) = K_1 e^{-2t} + K_2 e^{-3t} \quad \text{and} \quad v_C(t) = 100 + K_1 e^{-2t} + K_2 e^{-3t} \text{ V}$$

We have

$$v_C(0^-) = 80 \text{ V} \quad \text{and} \quad i_C(0^-) = C \left. \frac{dv_C}{dt} \right|_{0^-} \implies \dot{v}_C(0^-) = \frac{0.2}{1/120} = 24 \text{ V}$$

## RLC Circuit: Hard Example II

Thus

$$100 + K_1 + K_2 = 80 \quad \text{and} \quad -2K_1 - 3K_2 = 24$$

$$K_1 = -36, \quad K_2 = 16$$

We obtain

$$v_C(t) = 100 - 36e^{-2t} + 16e^{-3t} \text{ V}$$

# Reference

1. William H. Hayt, Jr., Jack E. Kemmerly, and Steven M. Durbin *Engineering Circuit Analysis*, 8th Edition McGraw-Hill, 2012.
2. J. David Irwin, and R. Mark Nelms *Basic Engineering Circuit Analysis*, 11th, Wiley, 2015.