

**Instruction:** This is an online exam.

Member:

1. Name: \_\_\_\_\_ Code: \_\_\_\_\_

**Questions:** Your answer sheet is a Microsoft word file which has `s+studentID.docx` as your file name. You also ask to work on a sheet of paper to show your solutions. The later can submit in any form

1 Download two files, namely `exam_2020.mat` and `fourier_p2exam.m`, and do the following tasks:

(a) run `fourier_p2exam.m` on your Matlab workspace and see the results.

(b) From the plot, you can change the Matlab code or using your hand to find  $a_3$  and  $b_5$ , which are two of the Fourier series coefficients. Write down the value of  $a_3$  and  $b_5$  on your answer sheet. (10 points)

2 Find the Fourier Transform of

$$f(t) = 5 + K\sqrt{2}e^{-1} \cos(t - 135^\circ), \quad (1)$$

where  $K$  is your last digit number of your student ID. Type your answer in your answer sheet. (10 points)

3 From the Figure 1 Find the transfer function from  $x(t)$  to  $y_1(t)$  and  $x(t)$  to  $y_2(t)$ . Write

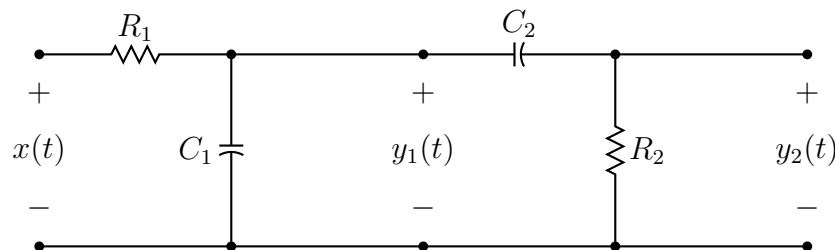


Figure 1: RC circuit

down you answer in your answer sheet. (10 points)

4 Consider a signal

$$x(t) = 5 \cos(10\pi t) + \sin(90\pi t)$$

shown in Figure 2. If we consider a part of the signal  $x(t)$  that has a frequency lower

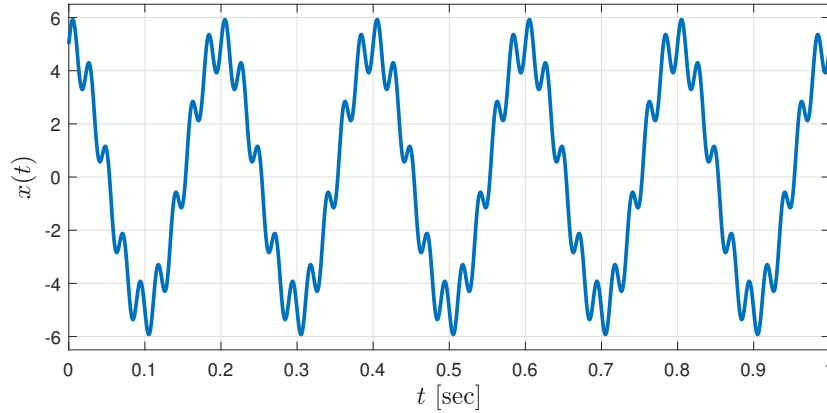


Figure 2: A sinusoidal signal

than  $90\pi$  rad/sec is a noise. Using a RC circuit to construct a high-pass filter. What is a cut-off frequency? If we select  $R = 1 \text{ k}\Omega$ , what is your design value of  $C$  to extract the signal  $y(t) = \sin(90\pi t)$ . Write down your answer in the answer sheet. (10 points)