

Instruction: This is an in class assignment.

Member:

1. Name: _____ Code: _____

Questions: Low-Pass Filter

1. Consider a signal

$$x(t) = 5 \cos(10\pi t) + \sin(90\pi t)$$

shown in Figure 1. If we consider a part of the signal $x(t)$ that has a frequency greater

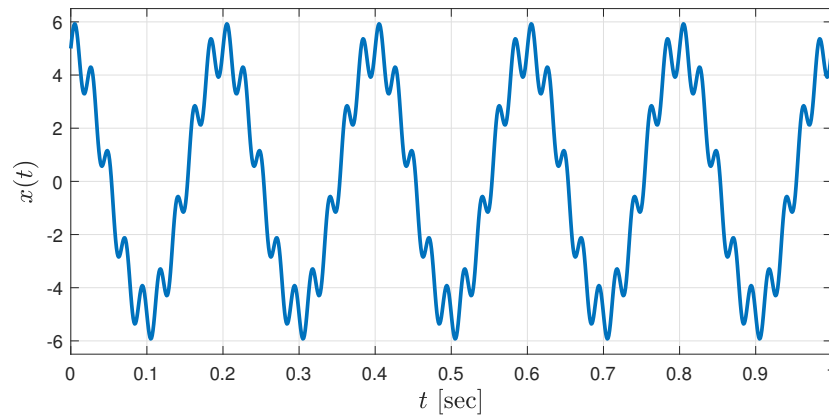


Figure 1: A sinusoidal signal

than 10π rad/sec is a noise. Using a RC circuit in Fig 2, design values of R and C to extract the signal $y(t) = 5 \cos(10\pi t)$. Show your analysis in terms of the filter design studied in class, and plot of $x(t)$ and $y(t)$ on the same axis. The best design will get 10 points. If we have n duplicated design, the score will divide with n .

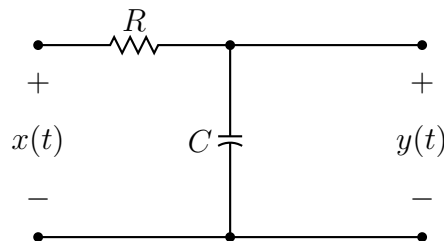


Figure 2: RC circuit