

Basic DC Power Supply

Equipment:

1. Oscilloscope
2. Digital multimeter
3. Experimental board and connectors.

Objectives:

1. To understand the basic DC power supply both half wave and full wave rectifier.
2. To understand the filter and the regulator circuit.
3. To understand the effect of load.

Cautions This is power supply lab. Lot of power will be delivered to Load (R_L) via diode. These components will become very **HOT**. Don't touch them.

1. Half Wave Rectifier Circuit

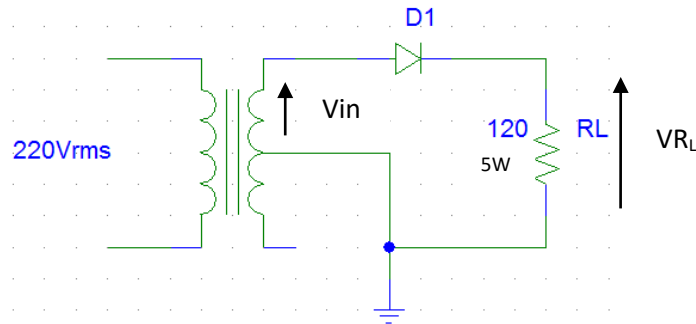


Fig.1

Calculate voltage across load (R_L), average voltage, average current and peak inverse voltage and plot the voltage across load (R_L)

.....

.....

.....


.....

.....

.....


.....

.....

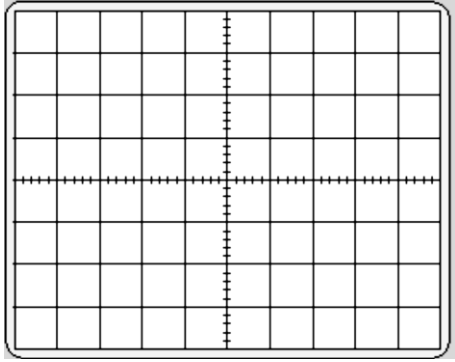


V_{R_L} Volt/Div _____ Time/Div _____

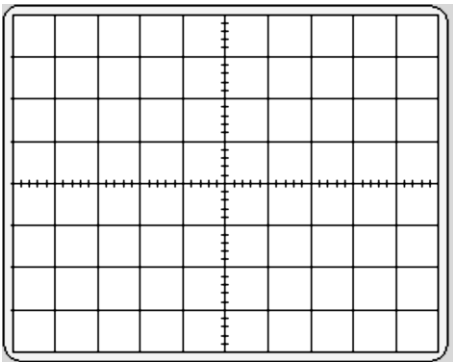Build the circuit as shown in Fig.1 and use oscilloscope to measure and record waveforms.




V_{in} Volt/Div _____ Time/Div _____

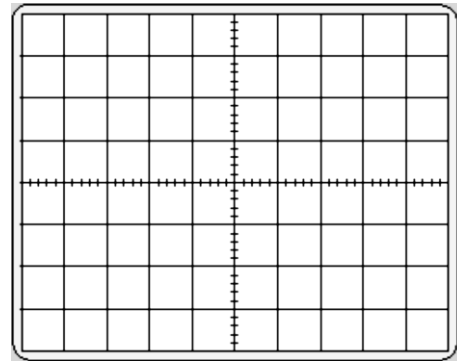

V_{R_L} Volt/Div _____ Time/Div _____


Measure the voltage across load (R_L) with digital multimeter (DC mode) = _____ Volt.

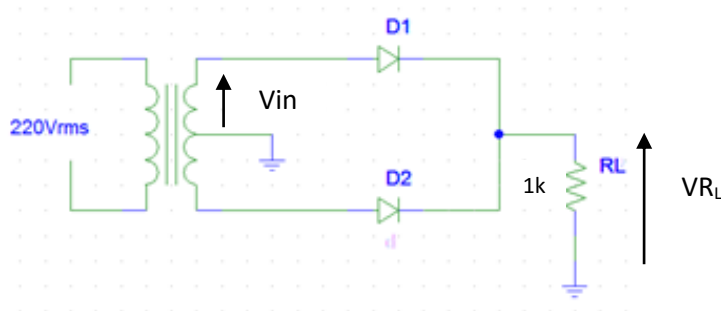2. Center Tapped Full wave rectifier circuit




Calculate voltage across load (R_L), average voltage, average current and peak inverse voltage and plot the voltage across load (R_L)

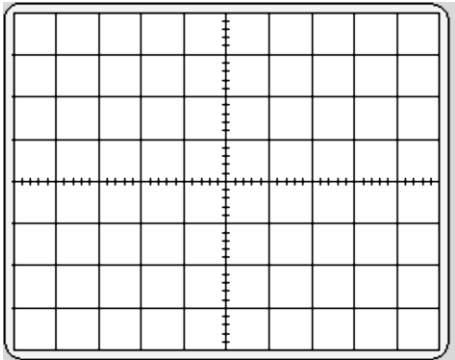.....
.....
.....
.....
.....
.....
.....
.....




V_{R_L} Volt/Div _____ Time/Div _____

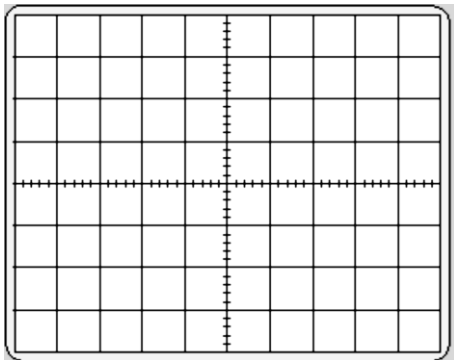Build the circuit and use oscilloscope to record waveforms.




V_{in} Volt/Div _____ Time/Div _____

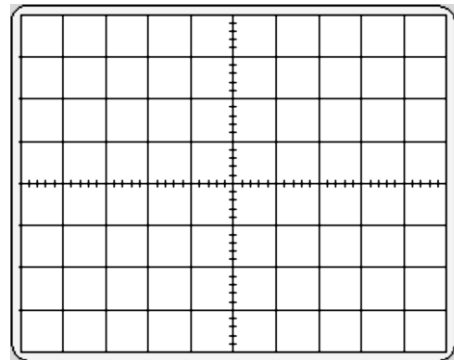

V_{R_L} Volt/Div _____ Time/Div _____

Measure the voltage across load (R_L) with digital multimeter (DC mode) = _____ Volt.

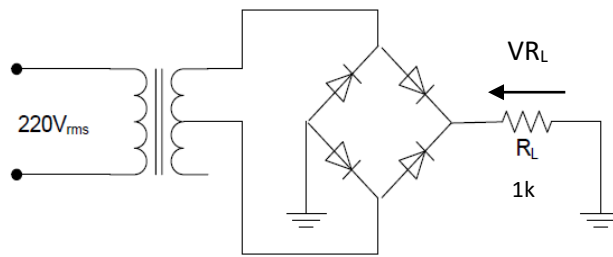3. Bridge Full wave rectifier circuit (Don't measure V_{in})



Calculate voltage across load (R_L), average voltage, average current and peak inverse voltage and plot the voltage across load (R_L)

.....

.....

.....

.....


.....

.....

.....


.....

.....

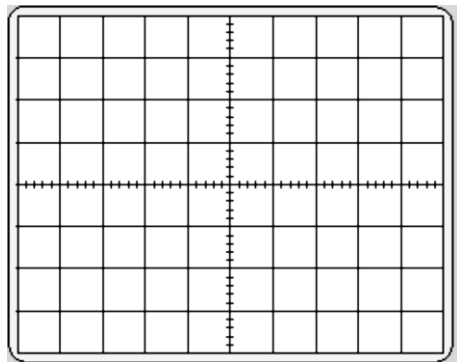


V_{R_L} Volt/Div _____ Time/Div _____

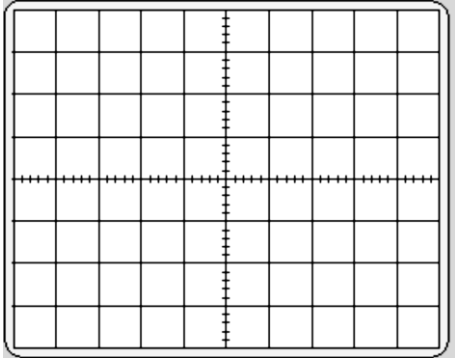Build the circuit and use oscilloscope to record waveforms.




V_{R_L} Volt/Div _____ Time/Div _____

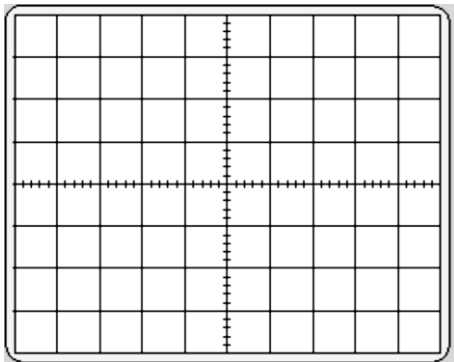Build the circuit and use oscilloscope to record waveforms.




V_{in} Volt/Div _____ Time/Div _____

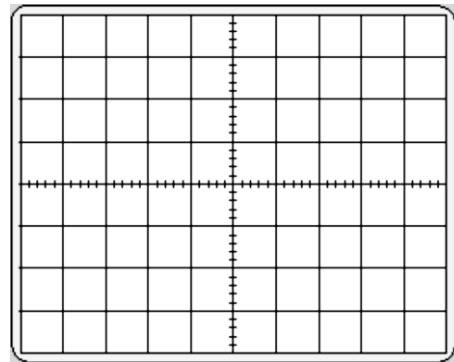


V_{R_L} Volt/Div _____ Time/Div _____

Measure the voltage across load (R_L) with digital multimeter (DC mode) = _____ Volt.

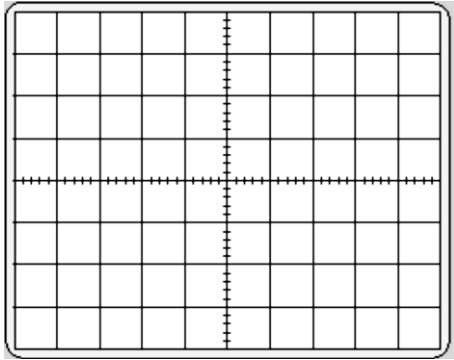Build the circuit and use oscilloscope to record waveforms.



V_{in} Volt/Div _____ Time/Div _____

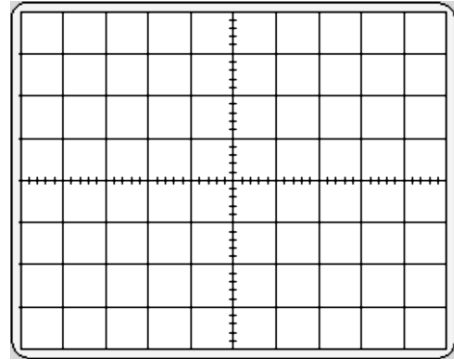

V_{R_L} Volt/Div _____ Time/Div _____

Measure the voltage across load (R_L) with digital multimeter (DC mode) = _____ Volt.

Revised by WL 28/10/2015

Lab Question: Determine the ripple factor for the filtered bridge rectifier with a load as indicate in this figure and show the voltage waveforms across R_L . Assume the secondary voltage of transformer is 15 V(RMS).

