



Filters

Contents




- Filters Types
- Basic Filter Responses
- Active Low-Pass Filters
- Active High-Pass Filters
- Active Band-Pass Filters
- Active Band-Stop Filters



Filter Types

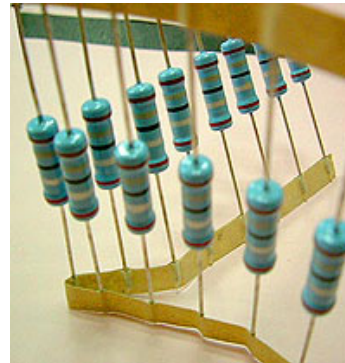- **Analog Filters**
- **Digital Filters**




- **Passive Filters:** uses passive R L C circuits
- **Active Filters:** uses Op-amps or transistors combined with passive R L C circuits
 - Active devices provide voltage gain
 - Passive R L C circuits provide frequency selectivity

Note. Active Filters require power supplies for operation.


Basic Filter Response



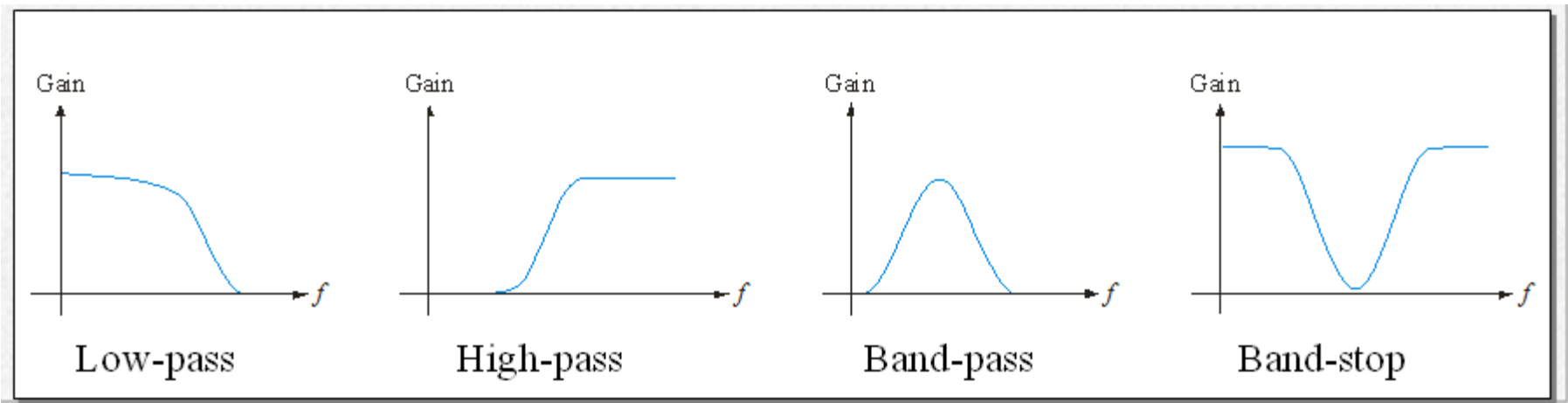
- **Filters** is a circuit that passes certain frequencies and attenuate or reject all other frequencies.
- **Passband** is the range of frequencies allowed through the filter.
- **The critical frequency, f_c** , also called *cutoff frequency* define the end of passband.(a point where the response drops -3dB or 70.7% from the passband response)




Low-pass filter response

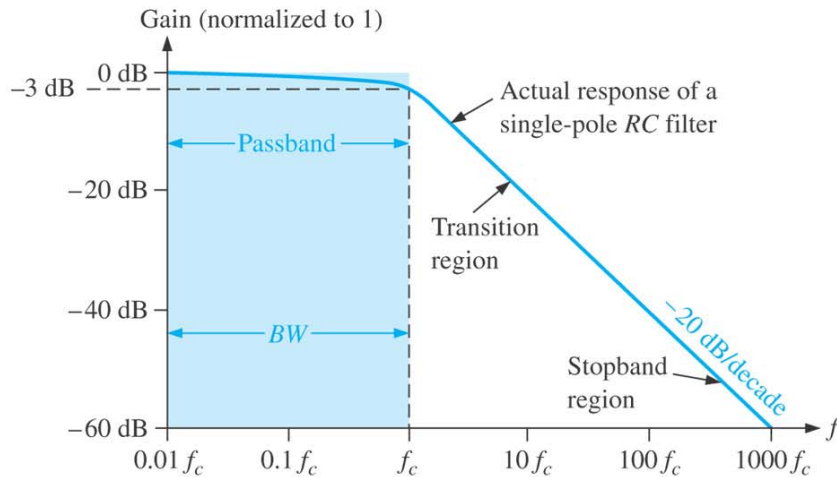

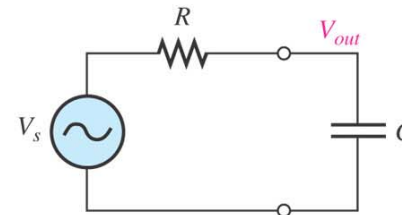(a) Comparison of an ideal low-pass filter response (blue area) with actual response



(b) Basic low-pass circuit

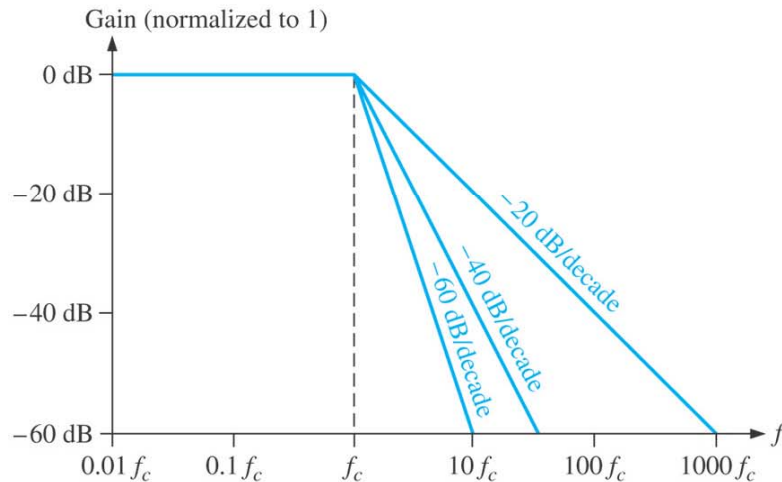


(c) Idealized low-pass filter responses


1. LP filter passes frequencies from dc to f_c .
2. Bandwidth(BW) = f_c
3. Poles: a circuit contained one R and C that contributes -20 dB/decade roll-off rate.

$$f_c = 1/2\pi RC$$


High-pass filter response

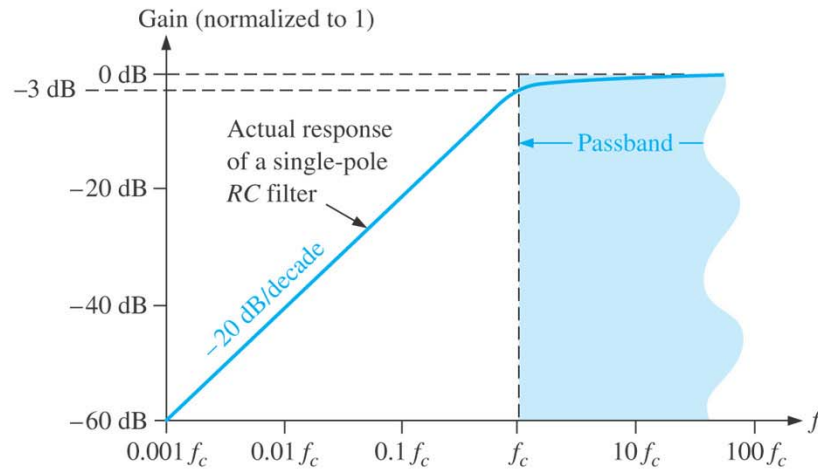

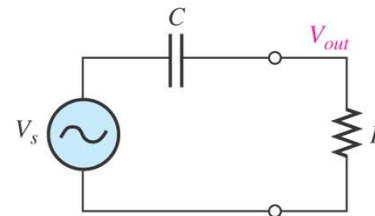(a) Comparison of an ideal high-pass filter response (blue area) with actual response



(b) Basic high-pass circuit

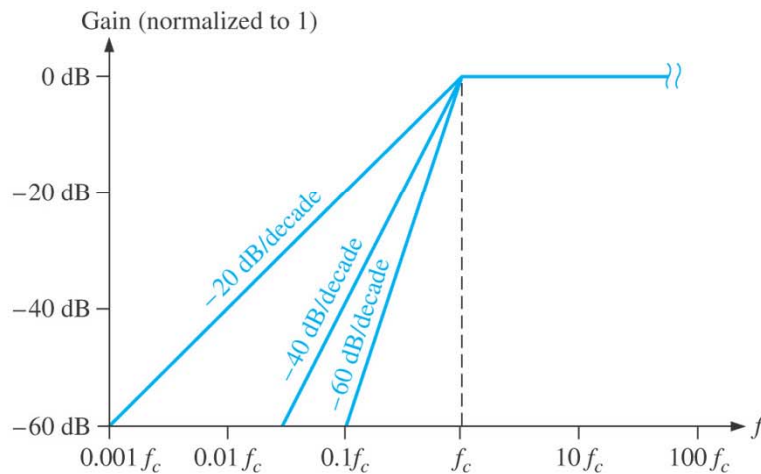


(c) Idealized high-pass filter responses

1. HP filter passes frequencies above f_c .
3. Poles: a circuit contained one R and C that contributes -20dB/decade roll-off rate.

$$f_c = 1/2\pi RC$$

Band-pass filter response

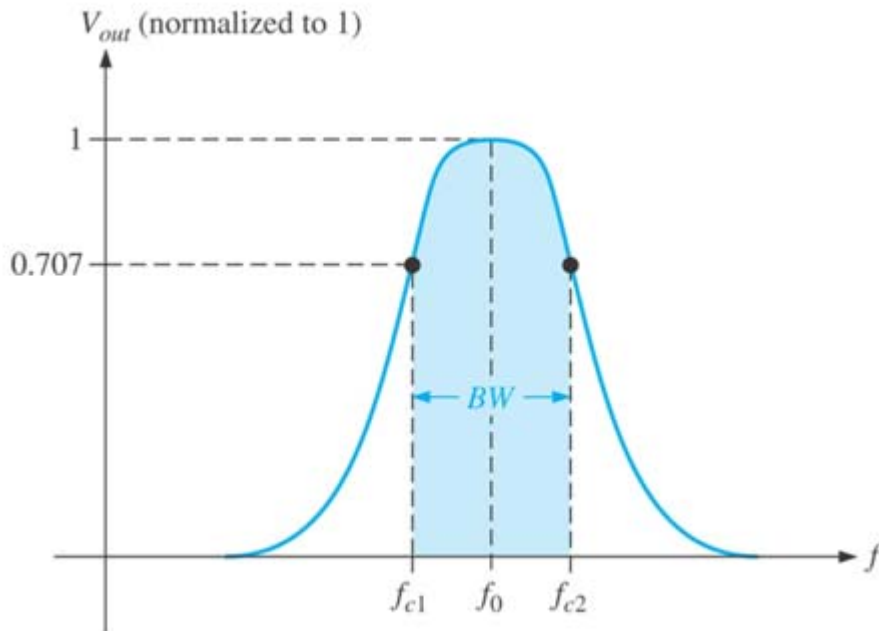


1. BP filter passes frequencies lying between f_{c1} and f_{c2} .
2. Bandwidth(BW) = $f_{c2} - f_{c1}$
3. The center frequency, f_0 is defined as;

$$f_0 = \sqrt{f_{c1}f_{c2}}$$

4. The quality factor(Q) is the ratio of f_0 to BW .

$$Q = \frac{f_0}{BW}$$

Band-stop filter response

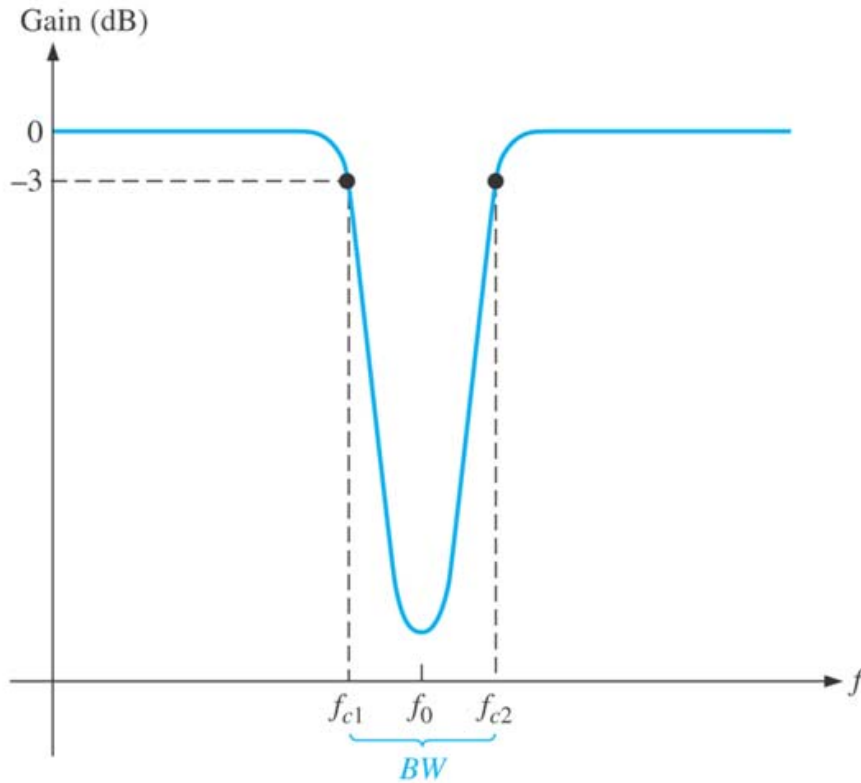

Also known as Notch, band-reject or band-elimination filter.

1. BS filter eliminates frequencies lying between f_{c1} and f_{c2} .
2. Bandwidth(BW) = $f_{c2} - f_{c1}$
3. The center frequency, f_0 is defined as;

$$f_0 = \sqrt{f_{c1}f_{c2}}$$

4. The quality factor(Q) is the ratio of f_0 to BW.

$$Q = \frac{f_0}{BW}$$