



---

# Bipolar Junction Transistor (BJT)

# Objectives




- To understand the structure of BJT.
- To explain and analyze the basic transistor circuits.
- To use transistors as an amplifier and electronic switch.
- To design the simple circuits using transistors.
- To study transistor parameters from datasheet.
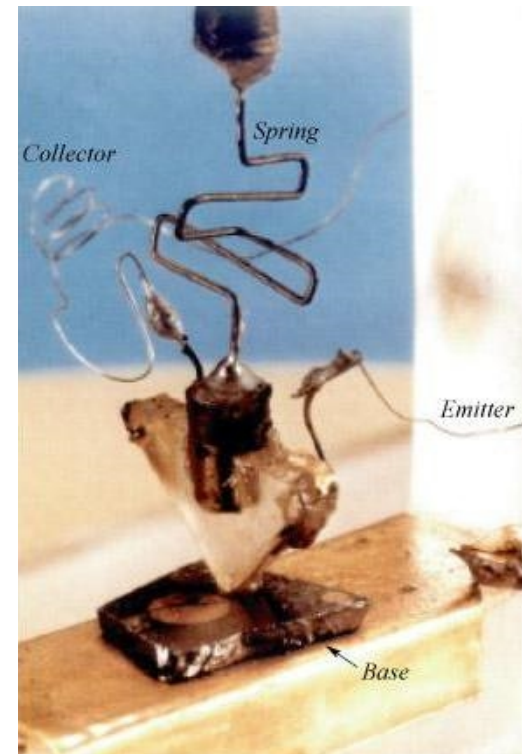
# What is Transistor?



- Invented in 1947 by John Bardeen, Walter Brattain and William Shockley
- Huge revolution in field of electronics
- First solid-state device able to amplify electric signal
- Universally used is Bipolar Junction Transistor(BJT)




Transistor in 1947


# Basic Functions




- Signal Amplifier
- Electronic Switch

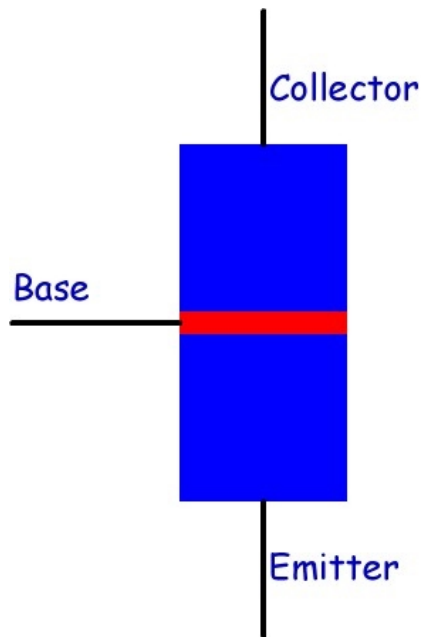

2 Types

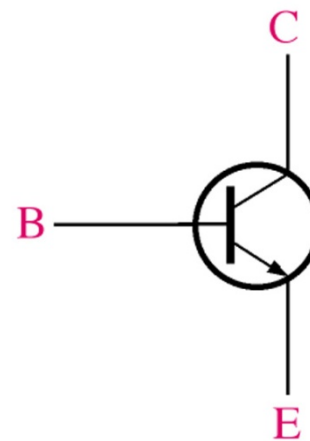

(a) *npn*

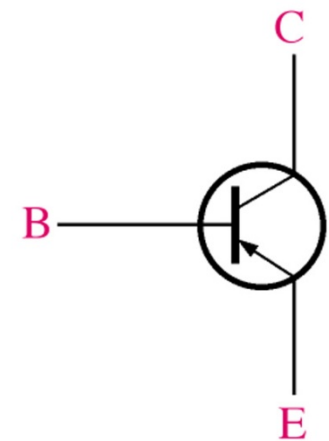


(b) *pnp*

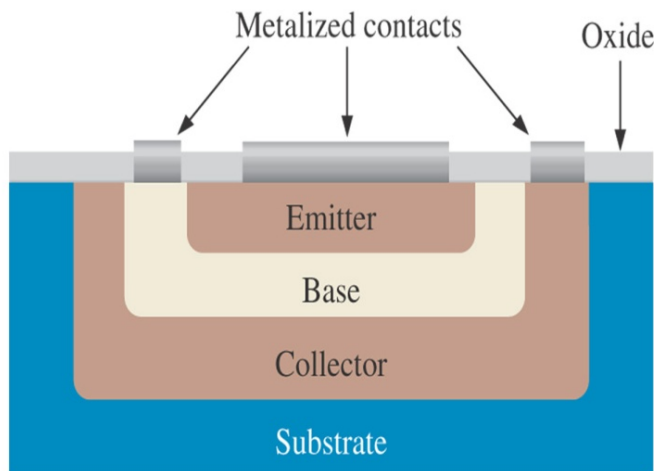
# Transistor Structure




With diodes there is one p-n junction. With **bipolar junction transistors (BJT)**, there are three layers and *two p-n junctions*.



(a) Basic epitaxial planar structure


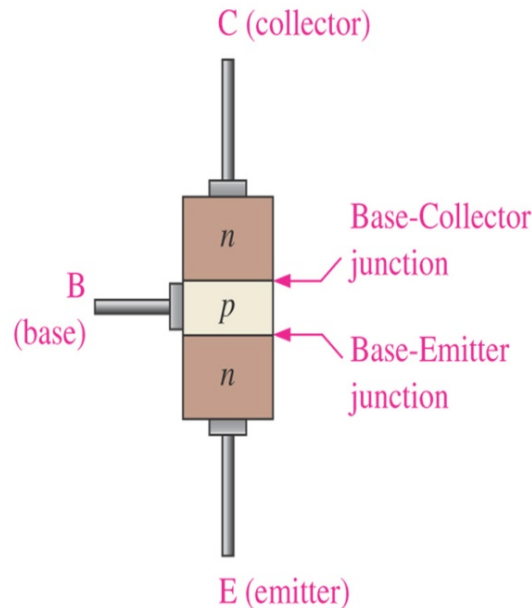


(b) npn

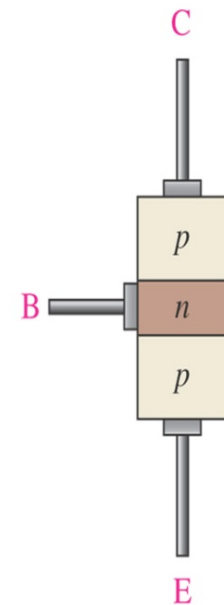


(c) pnp

# Conducting Current Direction

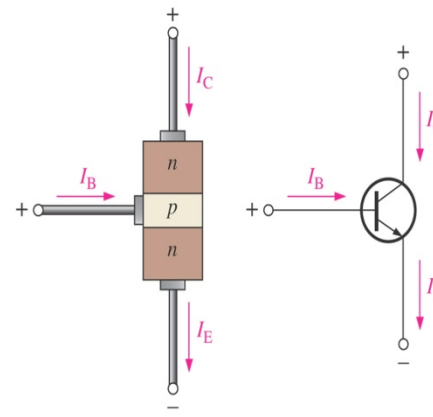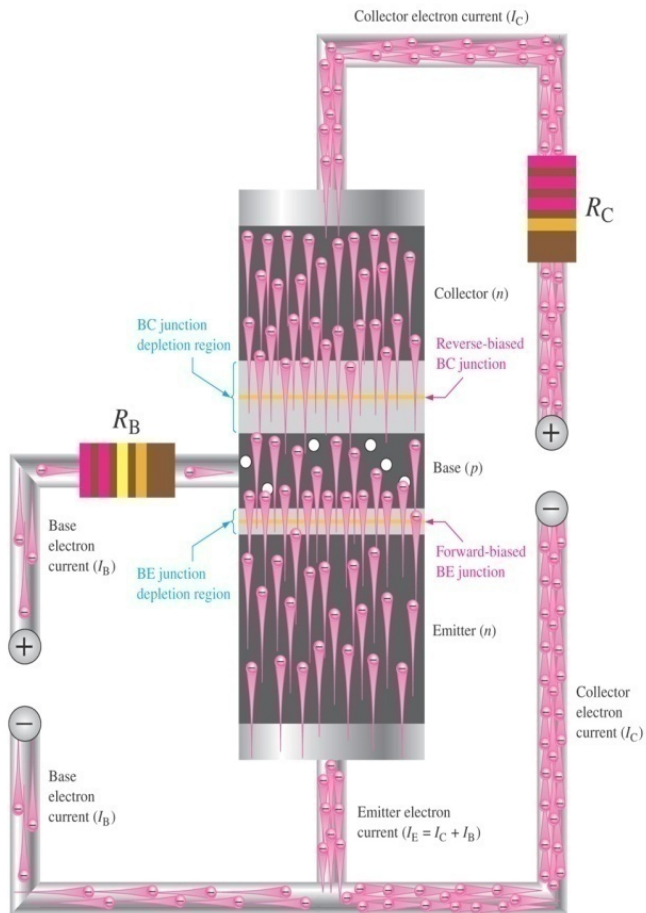

(a) *npn*

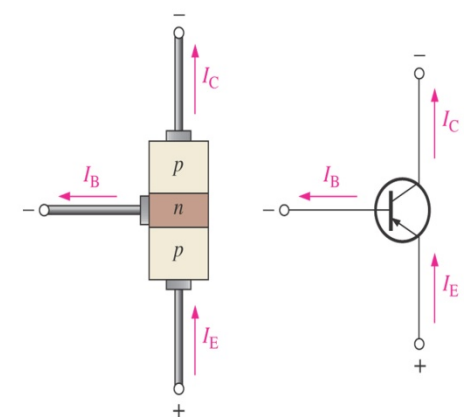


(b) *pnp*

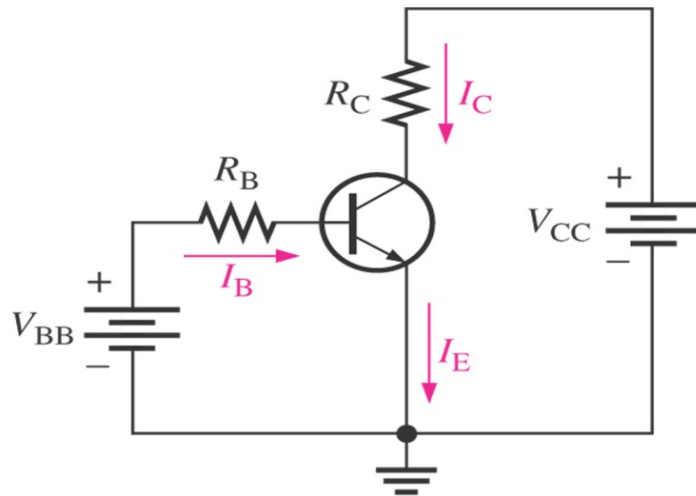
# Basic Operation



Look at this one circuit as two separate circuits, the base-emitter(left side) circuit and the collector-emitter(right side) circuit. Note that the emitter leg serves as a conductor for both circuits. The amount of current flow in the base-emitter circuit controls the amount of current that flows in the collector circuit. Small changes in base-emitter current yields a large change in collector-current.




(a) *npn*

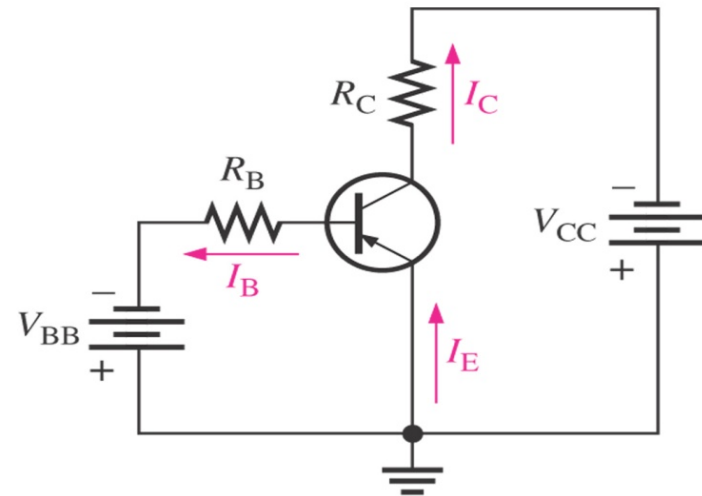

(b) *pnp*

# BJT Operation

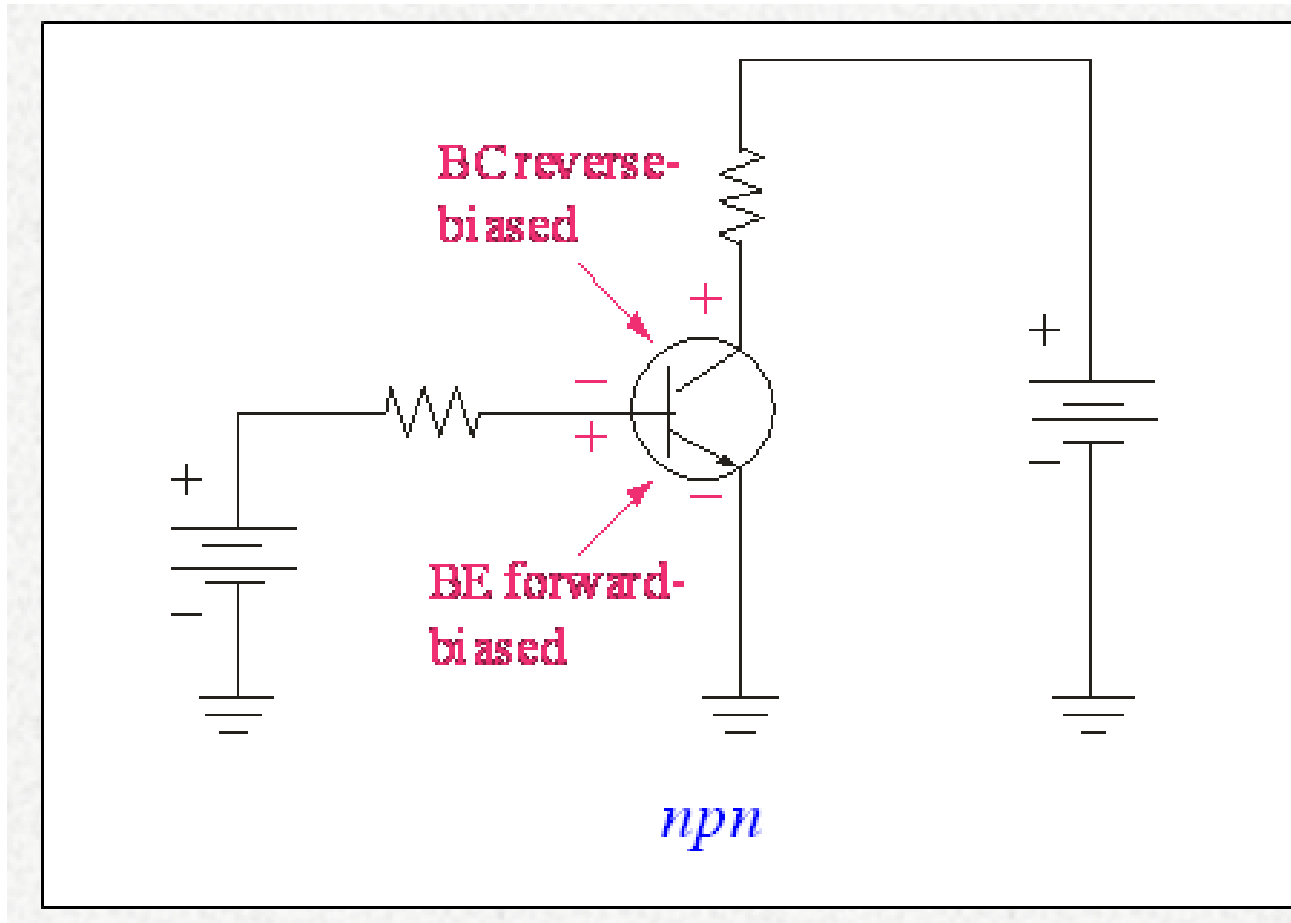




# Transistor Characteristics and Parameters



As previously discussed, base-emitter current changes yield large changes in collector-emitter current. The factor of this change is called **beta**( $\beta$ ).

$$\beta = I_C / I_B$$

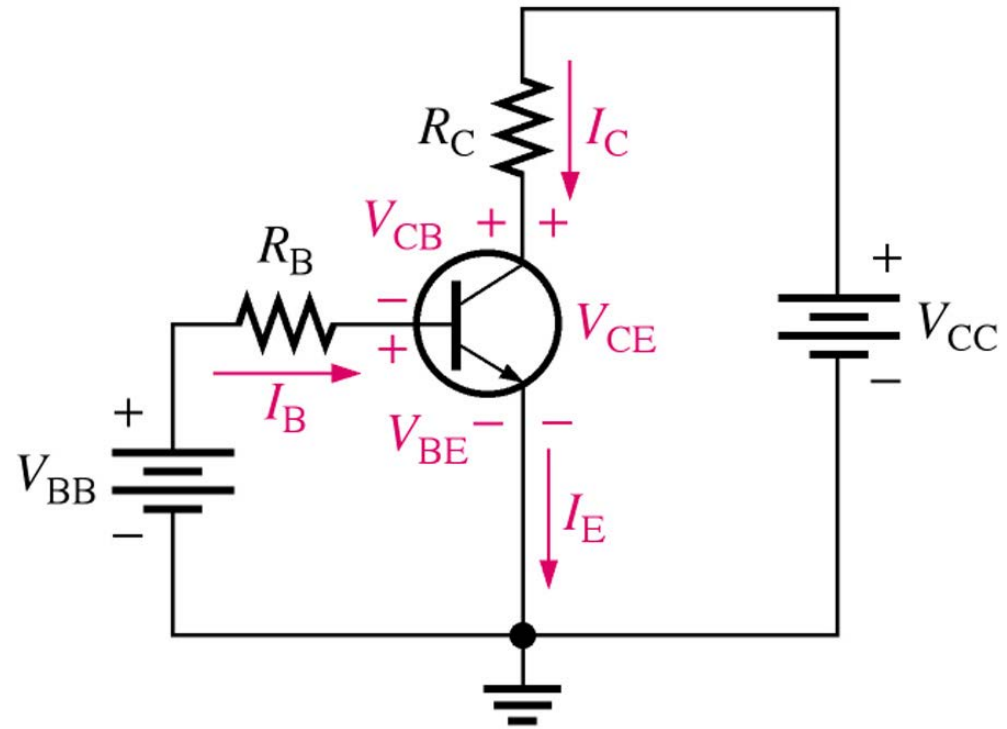

Common Emitter Configuration



---

The beta for a transistor is not always constant. Temperature and collector current both affect beta, not to mention the normal inconsistencies during the manufacture of the transistor.

There are also maximum power ratings to consider.

The data sheet provides information on these characteristics.



There are three key dc voltages and three key dc currents to be considered. Note that these measurements are important for troubleshooting.

$I_B$ : dc base current


$I_E$ : dc emitter current

$I_C$ : dc collector current

$V_{BE}$ : dc voltage across base-emitter junction

$V_{CB}$ : dc voltage across collector-base junction

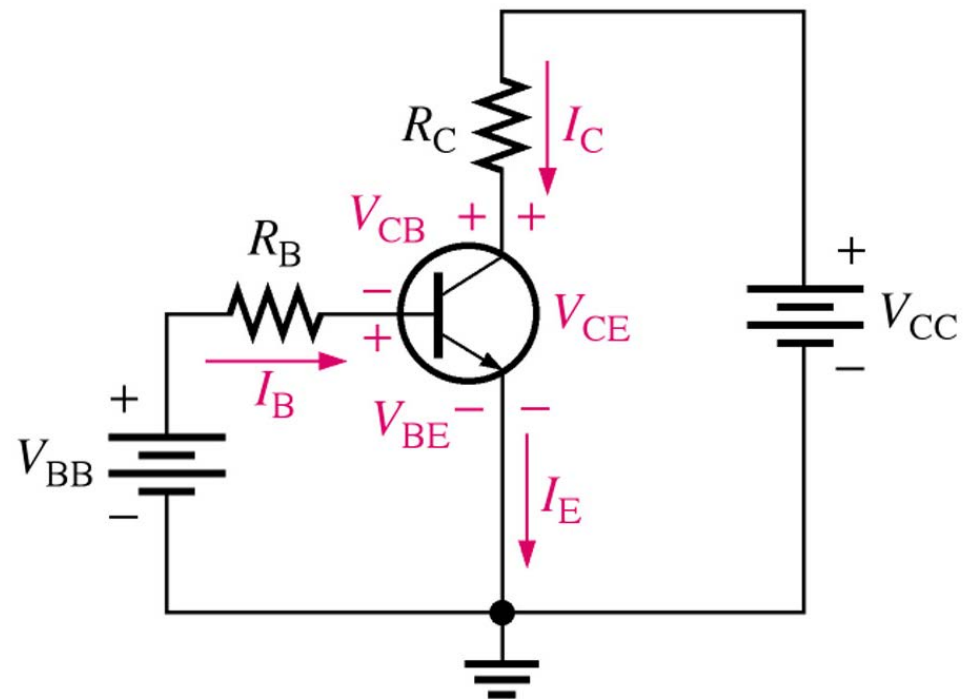$V_{CE}$ : dc voltage from collector to emitter






For proper operation, the base-emitter junction is forward-biased by  $V_{BB}$  and conducts just like a diode.

The collector-base junction is reverse biased by  $V_{CC}$  and blocks current flow through it's junction just like a diode.

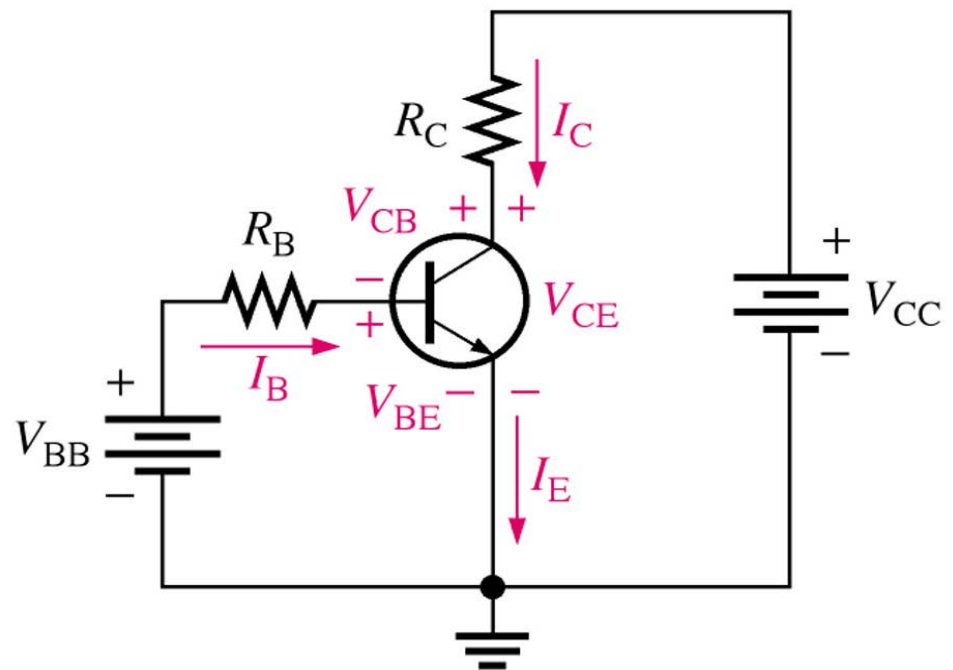Remember that current flow through the base-emitter junction will help establish the path for current flow from the collector to emitter.






Analysis of this transistor circuit to predict the dc voltages and currents requires use of Ohm's law, Kirchhoff's voltage law and the beta for the transistor.

Application of these laws begins with the base circuit to determine the amount of base current. Using Kirchhoff's voltage law, subtract the  $.7 V_{BE}$  and the remaining voltage is dropped across  $R_B$ . Determining the current for the base with this information is a matter of applying of Ohm's law.  $V_{RB}/R_B = I_B$

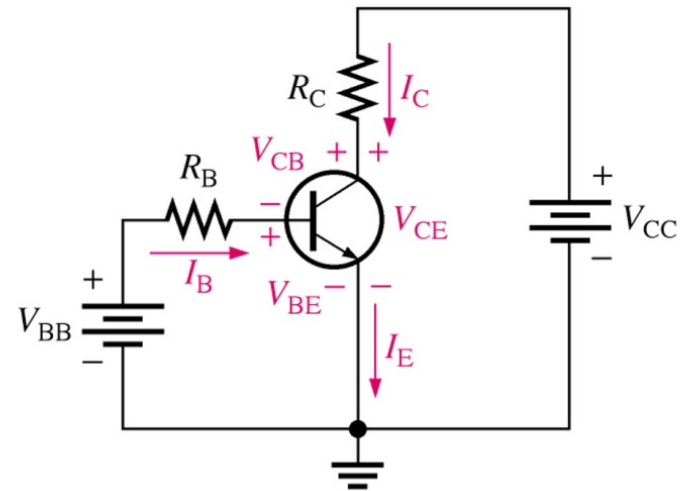
**The collector current is determined by multiplying the base current by beta.**




Note.  $V_{BE} = 0.7$  will be used in most analysis examples.



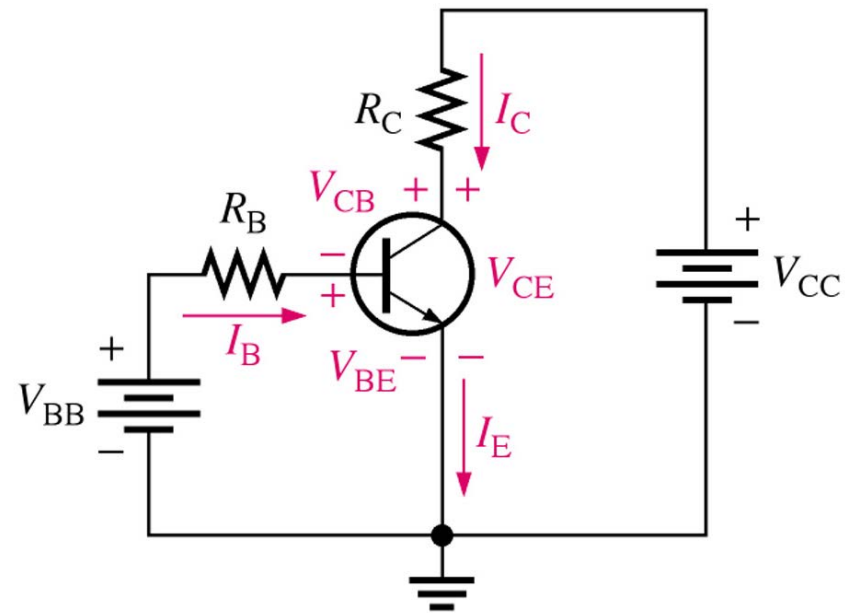What we ultimately determine by use of Kirchhoff's voltage law for series circuits is that in the base circuit  $V_{BB}$  is distributed across the base-emitter junction and  $R_B$  in the base circuit. In the collector circuit we determine that  $V_{CC}$  is distributed proportionally across  $R_C$  and the transistor ( $V_{CE}$ ).




# Three-transistor currents

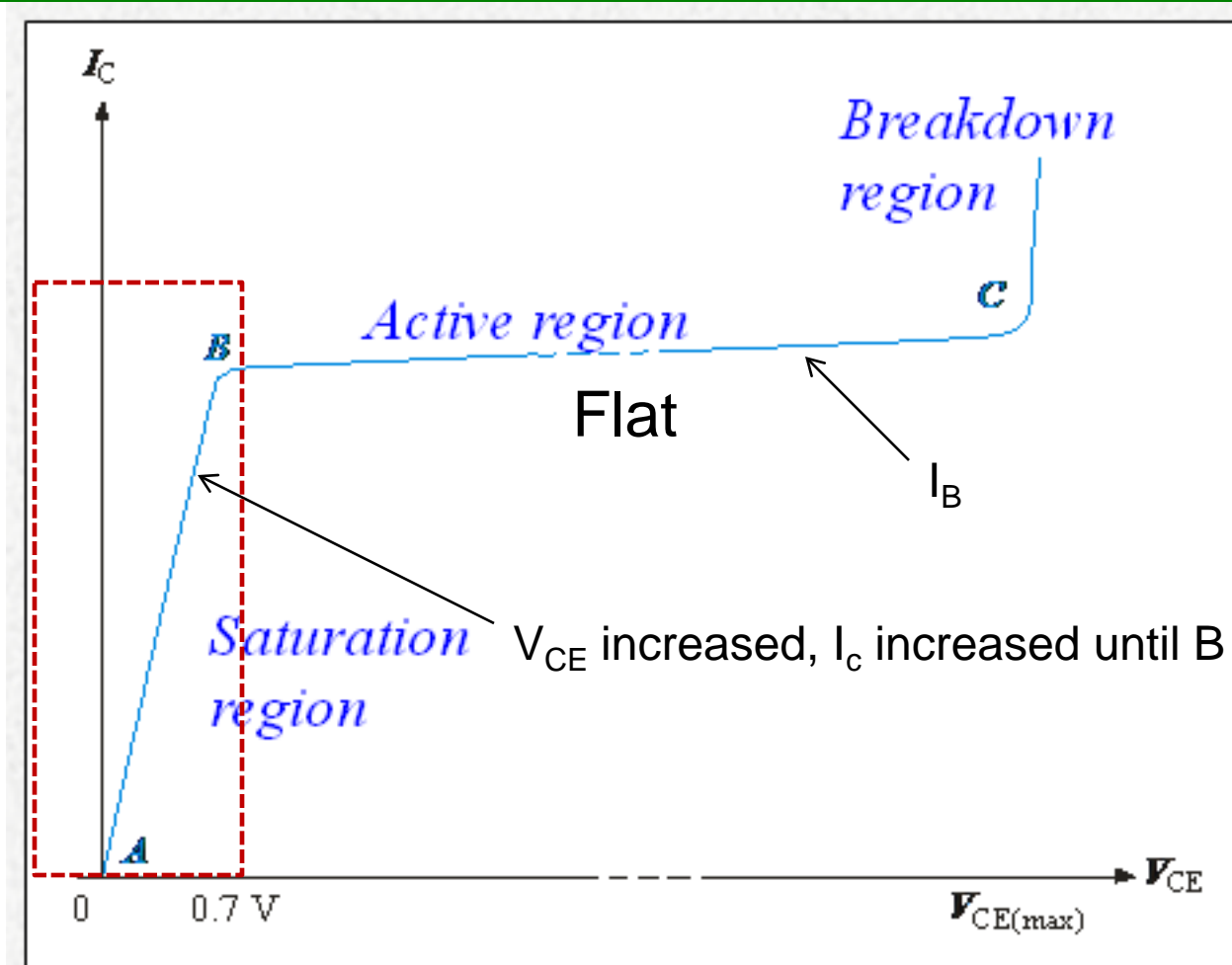

Curve shown for one fixed base current




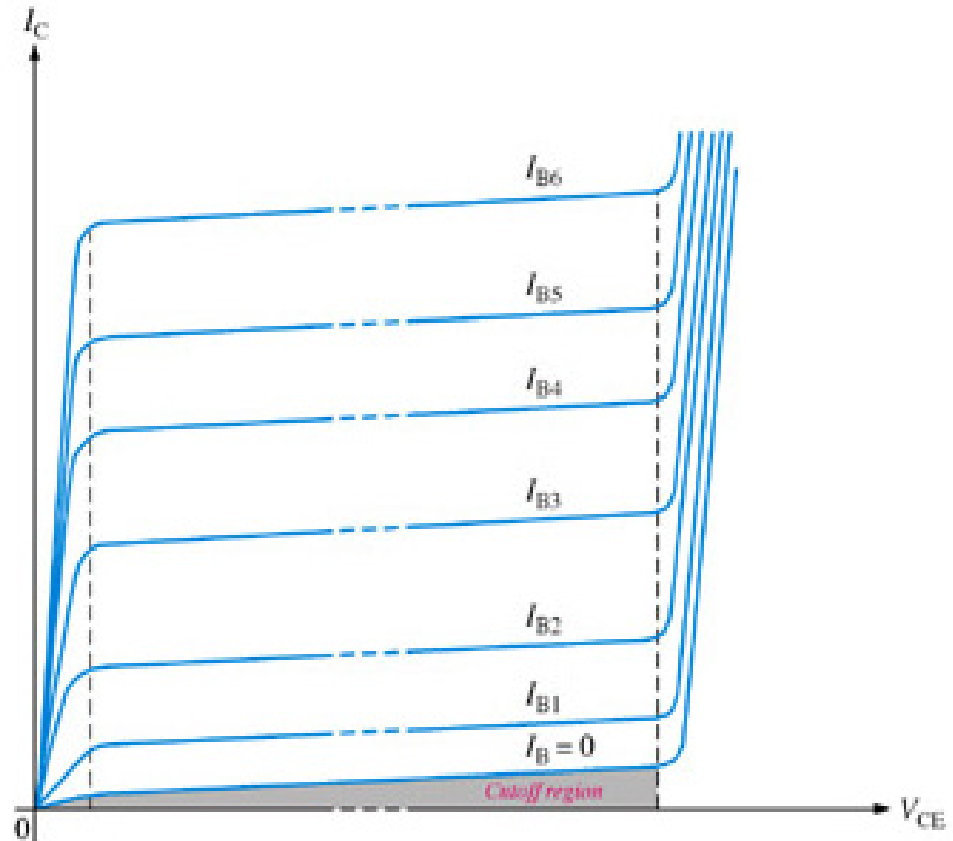**Collector characteristic curves** give a graphical illustration of the relationship of collector current and  $V_{CE}$  with specified amounts of base current. With greater increases of  $V_{CC}$ ,  $V_{CE}$  continues to increase until it reaches breakdown, but the current remains about the same in the **linear** region from .7V to the breakdown voltage.




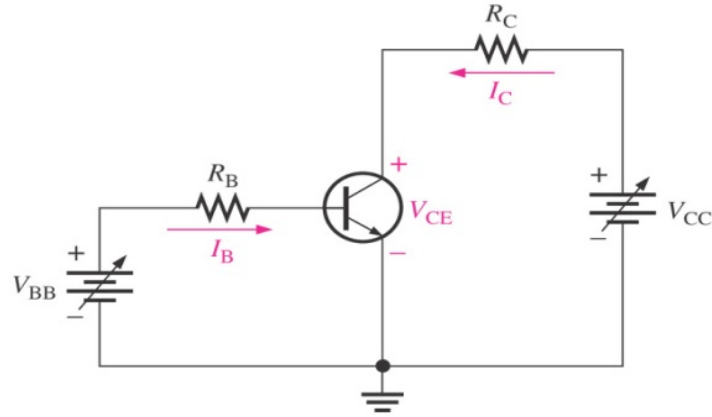(c) Family of  $I_C$  versus  $V_{CE}$  curves for several values of  $I_B$   
( $I_{B1} < I_{B2} < I_{B3}$ , etc.)






(a) Circuit

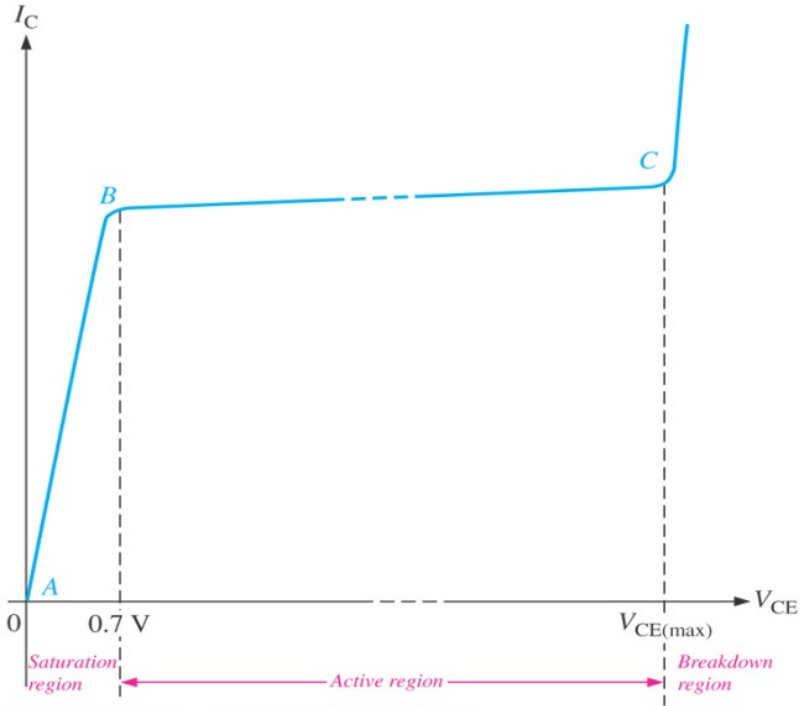

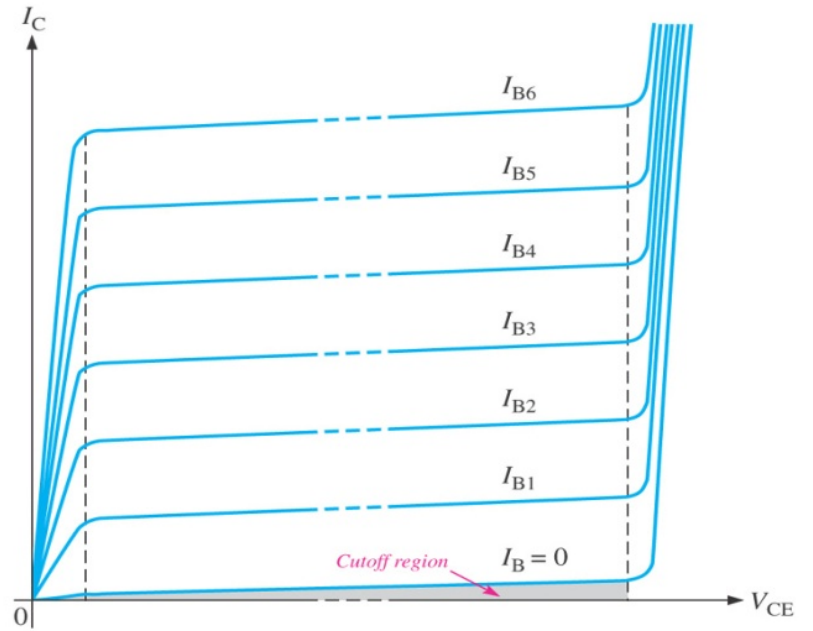(b)  $I_C$  versus  $V_{CE}$  curve for one value of  $I_B$





(c) Family of  $I_C$  versus  $V_{CE}$  curves for several values of  $I_B$  ( $I_{B1} < I_{B2} < I_{B3}$ , etc.)


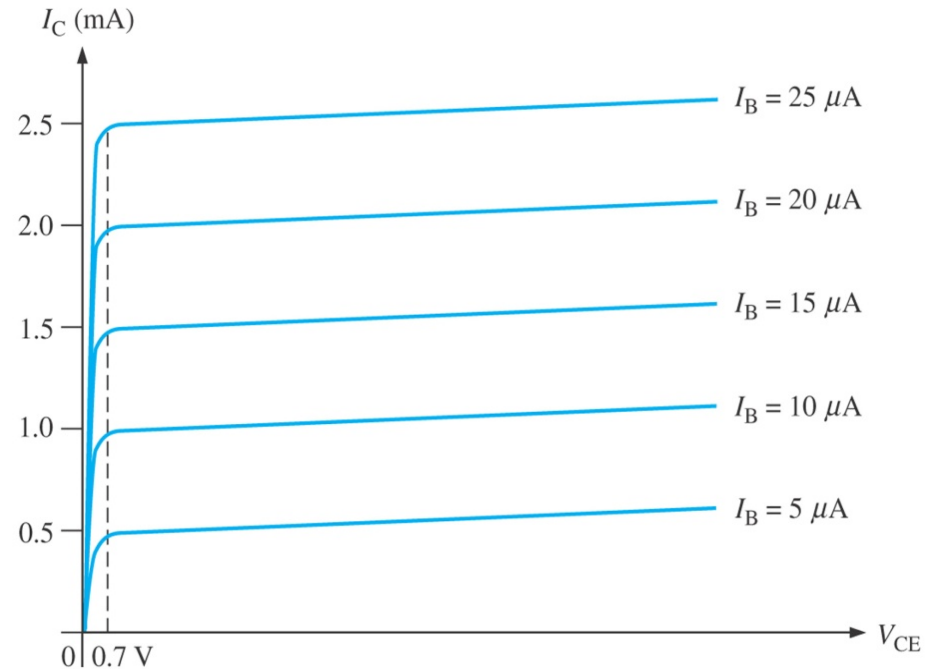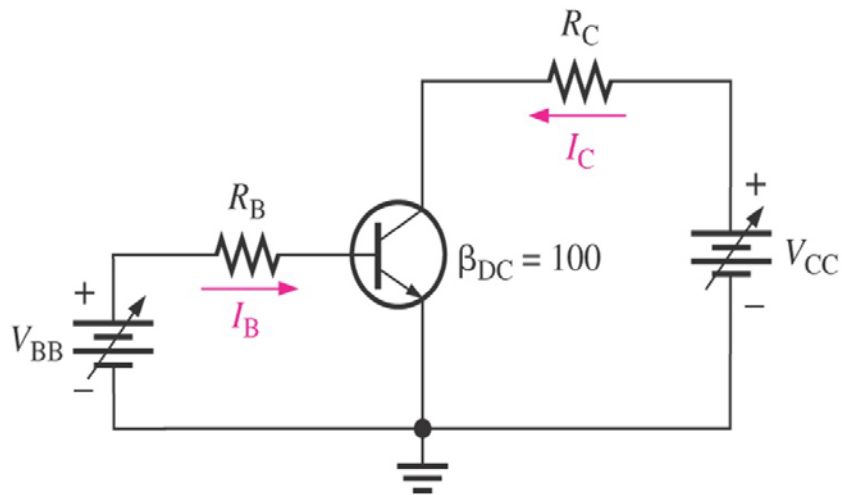
# Example

Sketch the transistor characteristic curve for  $I_B = 5\mu\text{A}$  to  $25\mu\text{A}$  with  $5\mu\text{A}$  increment  
Assume  $V_{CE}$  does not exceed breakdown.





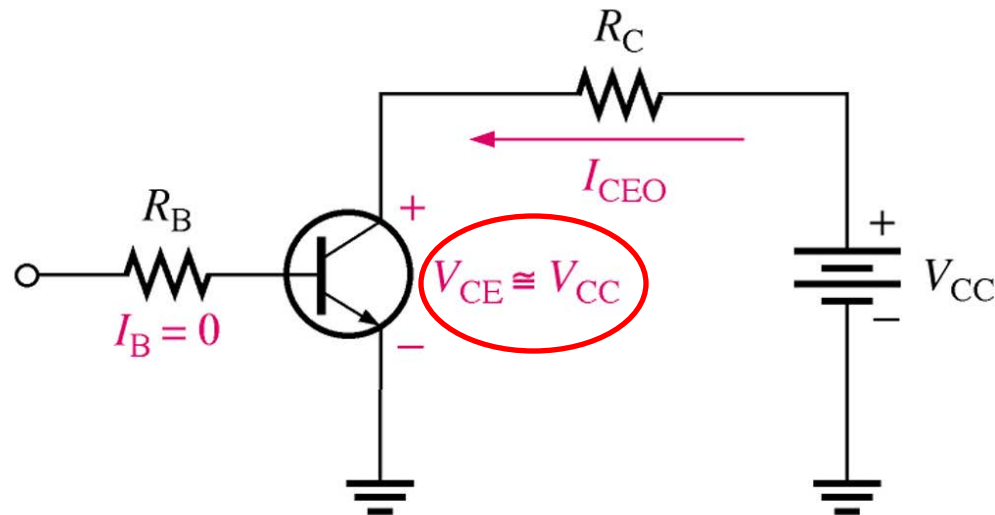
# Cut-off Mode



With no  $I_B$  the transistor is in the **cutoff** region and just as the name implies there is practically no current flow in the collector part of the circuit. This results in only an extremely small leakage current ( $I_{CEO}$ ) in the collector circuit. With the transistor in a cutoff state the full  $V_{CC}$  can be measured across the collector and emitter ( $V_{CE}$ ).




# Saturation Mode



Current flow in the collector part of the circuit is, as stated previously, determined by  $I_B$  multiplied by  $\beta$ . However, *there is a limit to how much current can flow in the collector circuit regardless of additional increases in  $I_B$ .* Once this maximum is reached, the transistor is said to be in **saturation**. Note that saturation can be determined by application of Ohm's law,  $I_{C(\text{sat})} = (V_{CC} - V_{CE}) / R_C$ . For Ideal case, the measured voltage across the now "**shorted**" collector and emitter ( $V_{CE}$ ) is 0V. The practical value is around 0.2V

In saturation, an increase of base current has no effect on collector circuit and the relationship  $I_C = \beta \cdot I_B$  is no longer valid.

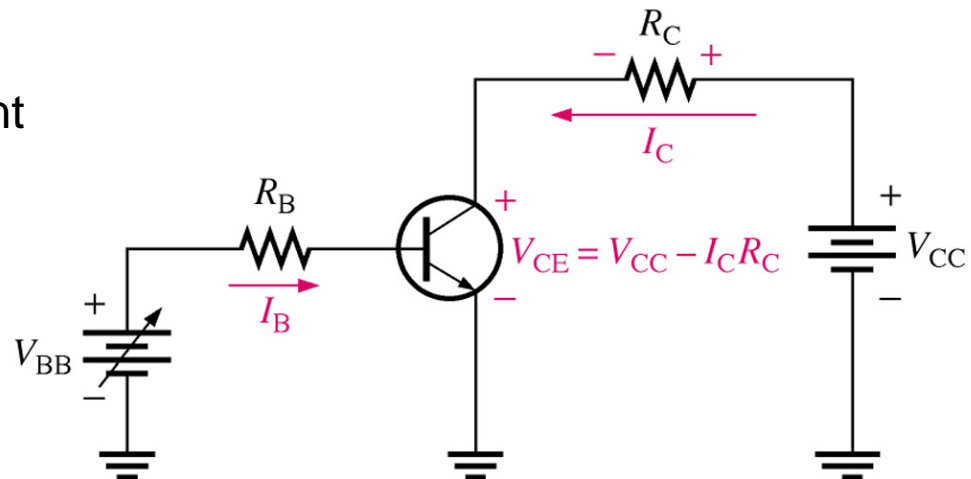


**Figure.** Saturation: As  $I_B$  increases due to increasing  $V_{BB}$ ,  $I_C$  also increases and  $V_{CE}$  decreases due to the increased voltage drop across  $R_C$ . When the transistor reaches saturation,  $I_C$  can increase no further regardless of further increase in  $I_B$ .
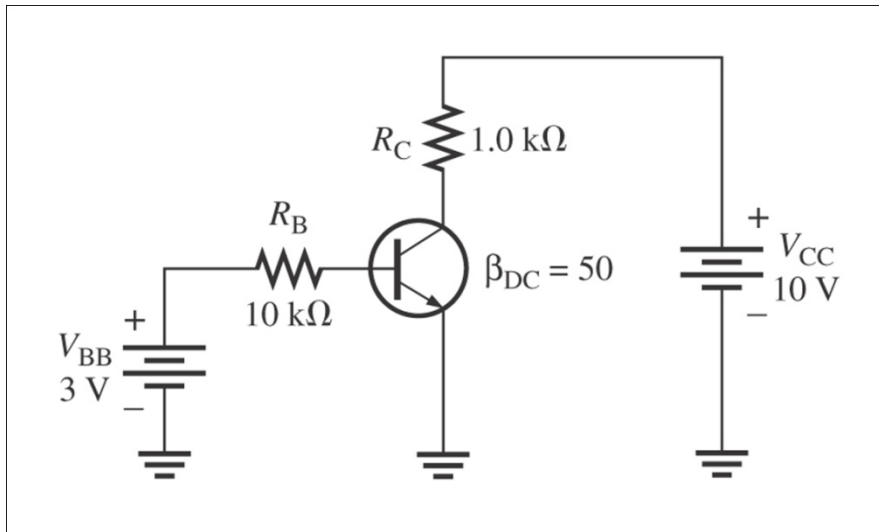
# Example



- Determine whether or not the transistor is in saturation. Assume  $V_{CE(sat)} = 0.2V$ .




# DC load line



The **dc load line** graphically illustrates  $I_{C(sat)}$  and cutoff for a transistor. Basically, dc load line represents the circuit which is external to transistor

KVL(Collector-Emitter)

$$V_{CE} = V_{CC} - I_C R_C$$

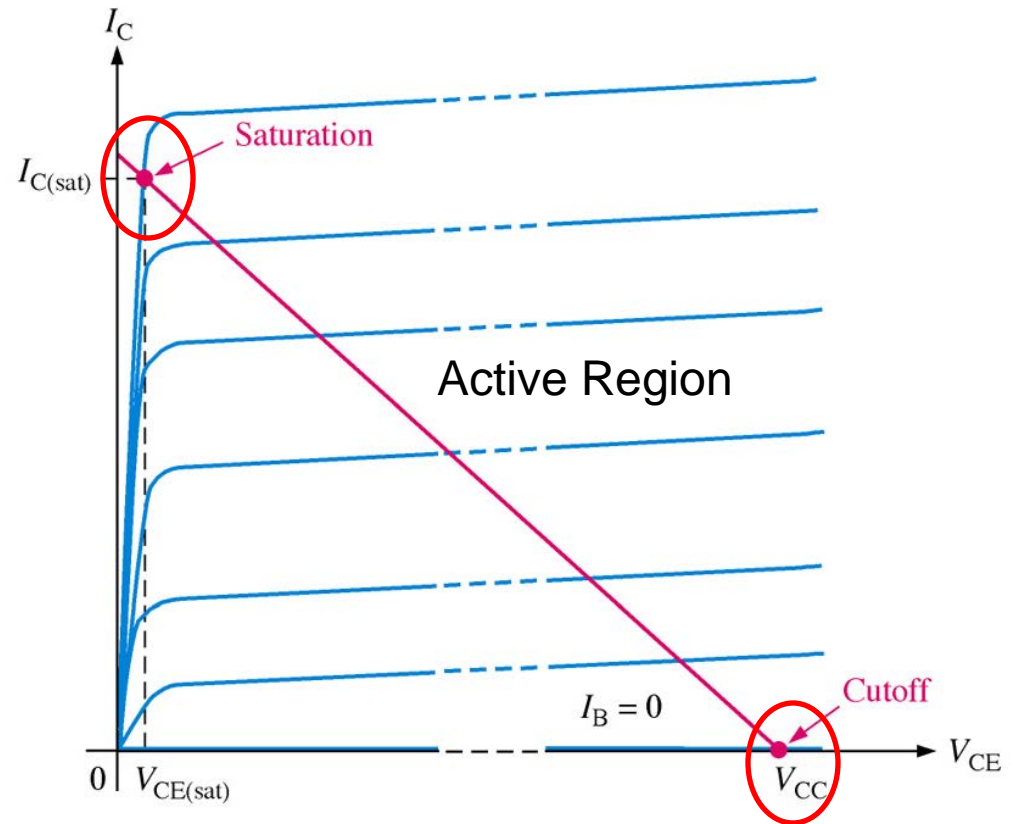


**Figure.** DC load line on a family of collector characteristic curves illustrating the cutoff and saturation conditions.
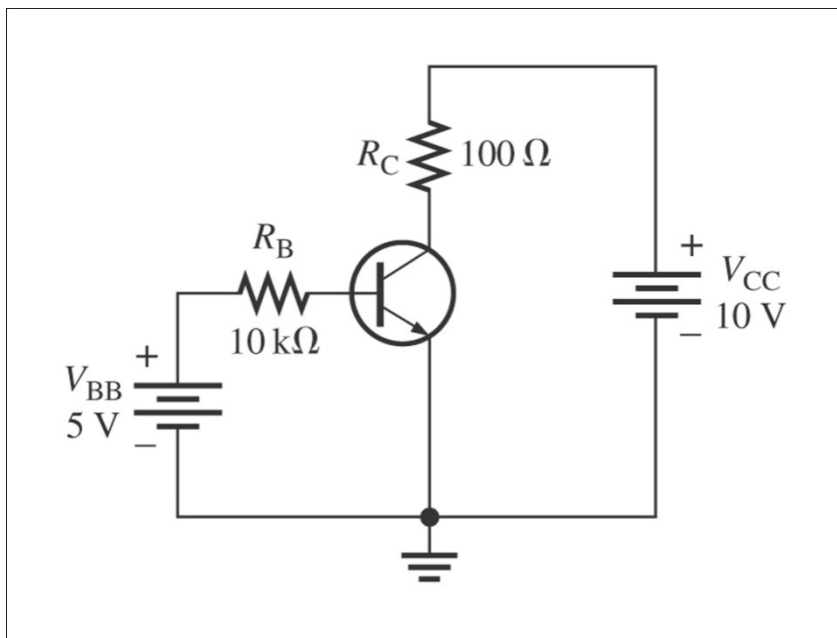
# Example



- From a given circuit, determine  $I_B$ ,  $I_C$ ,  $I_E$ ,  $V_{BE}$ ,  $V_{CE}$  and  $V_{CB}$ . The transistor has a  $\beta_{DC} = 150$ . Assume  $V_{CE(ON)} = 0.7V$ .







# Transistor as Amplifier




Amplification of a relatively small ac voltage can be had by placing the ac signal source in the base circuit.

Recall that small changes in the base current circuit causes large changes in collector current circuit.

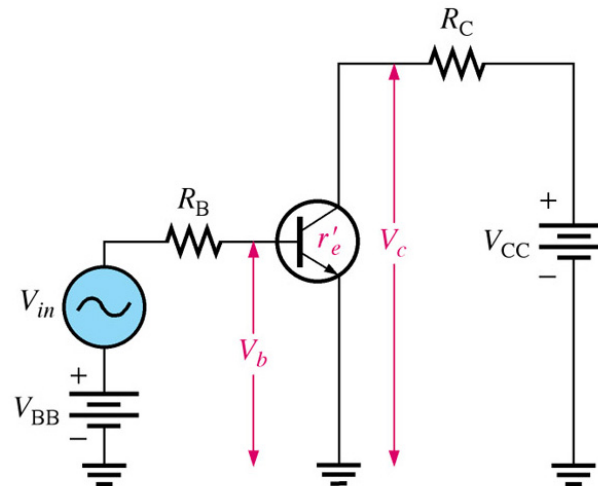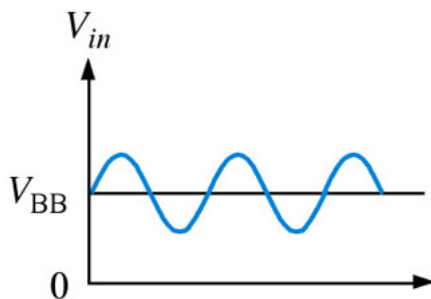The small ac voltage causes the base current to increase and decrease accordingly and with this small change in current the collector current will mimic the input only with **greater** amplitude.



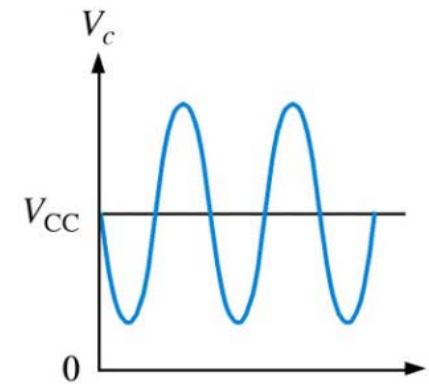(a) Circuit with ac input voltage  $V_{in}$  and dc bias voltage superimposed




(b) Waveforms

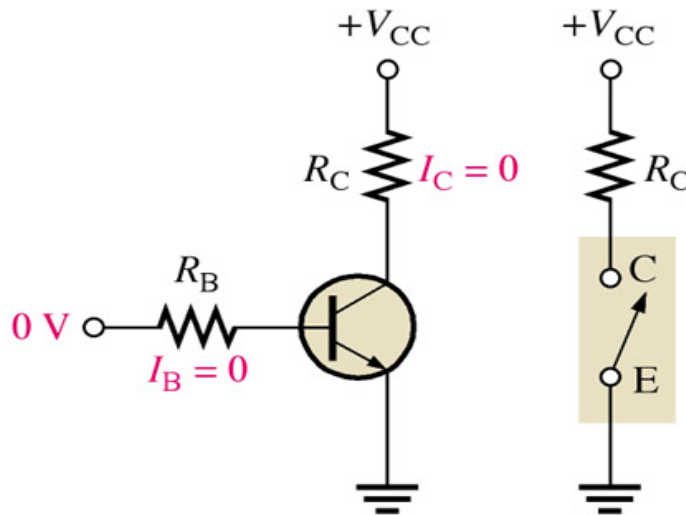
# Transistor as (Electronic) Switch



A transistor when used as a switch is simply being biased so that it is in cutoff (switched off) or saturation (switched on). Remember that the  $V_{CE}$  in cutoff is  $V_{CC}$  and 0 V in saturation.



(a) Cutoff — open switch


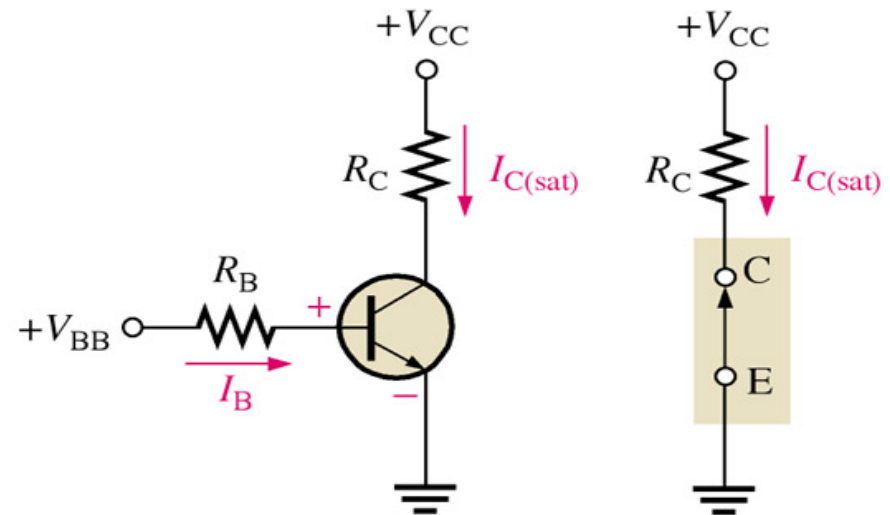


(b) Saturation — closed switch


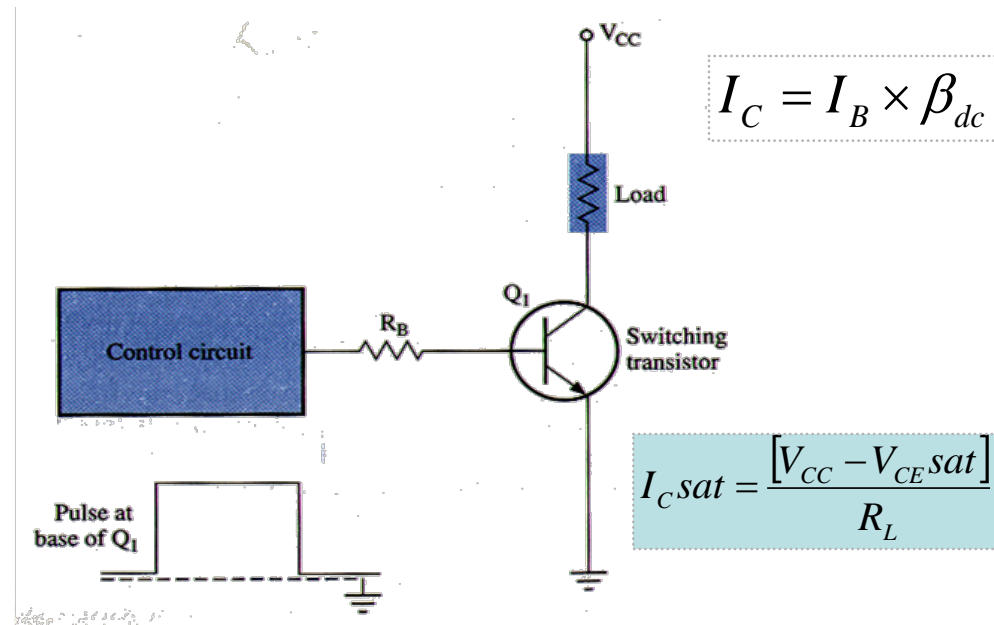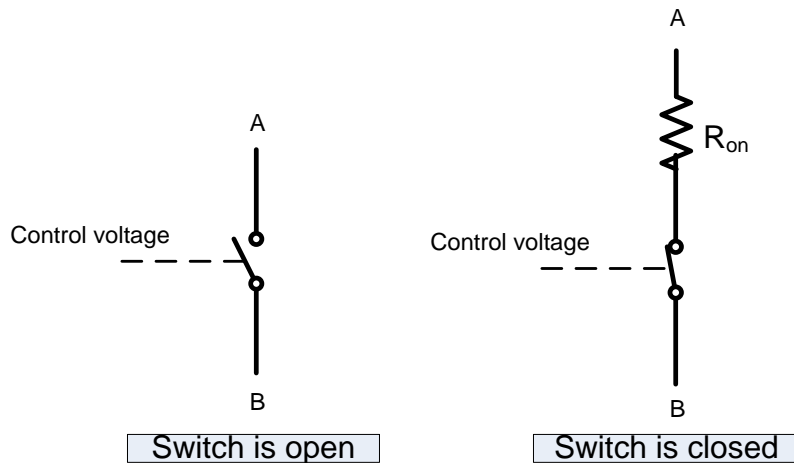
# Electronic Switch


- Electronic switch uses electrical control signal for operation.
- The electronic switch does not contain mechanical contacts but semiconductor devices such as bipolar junction transistors or field-effect transistors.
- For the design, input voltage should be selected such that the output is either completely off, or completely on i.e transistor works in **saturation mode**.



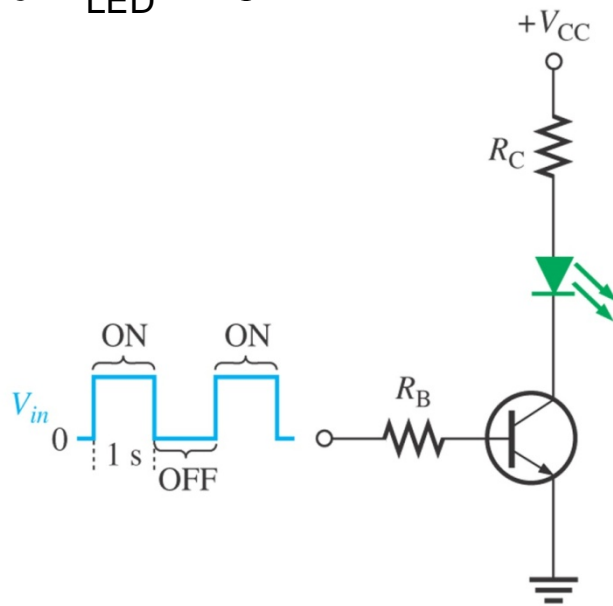
# Simple Application




The LED in a given circuit requires 30mA to emit a sufficient light. Determine the amplitude of square wave necessary to make sure the LED emit sufficient Light. Use double the minimum value of base current as a safety margin to ensure saturation.  $V_{CC}=9V$ ,  $V_{CE(SAT)}=0.3V$ ,  $R_C=220\Omega$ ,  $R_B=3.3k\Omega$ ,  $\beta_{DC} = 50$ , and  $V_{LED}=1.6V$ .



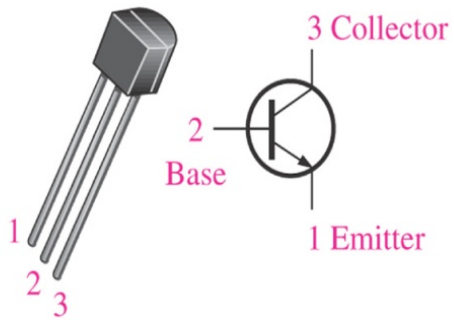
# Plastic cases for general-purpose/small-signal transistors.



(a) TO-92 or TO-226AA

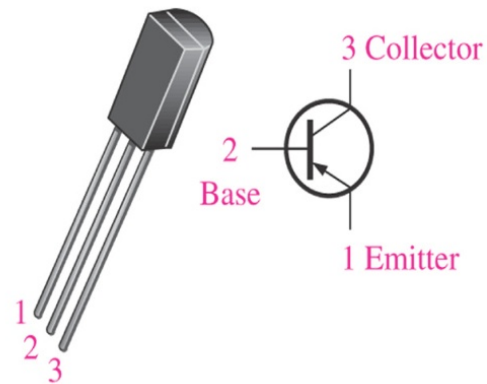


(b) TO-92 or TO-226AE

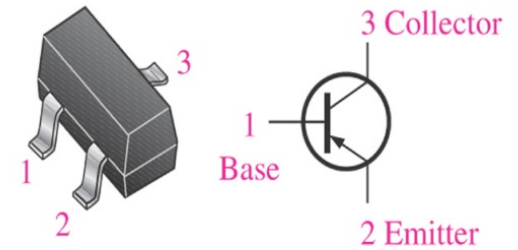


(c) SOT-23 or TO-236AB

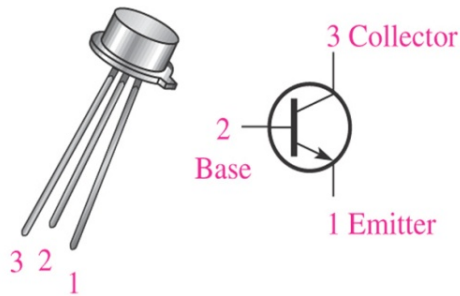
# Metal cases for general-purpose/small-signal transistors




(a) TO-18 or TO-206AA

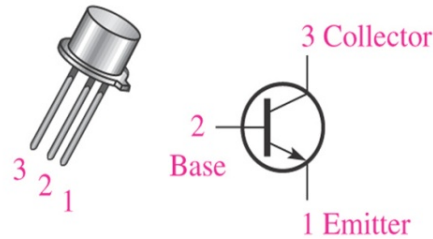


(b) TO-39 or TO-205AD

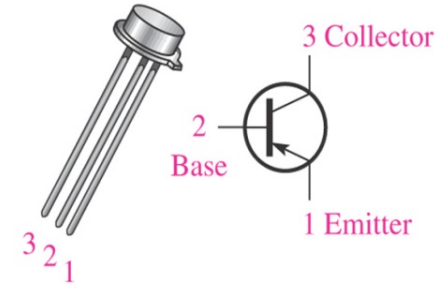


(c) TO-46 or TO-206AB

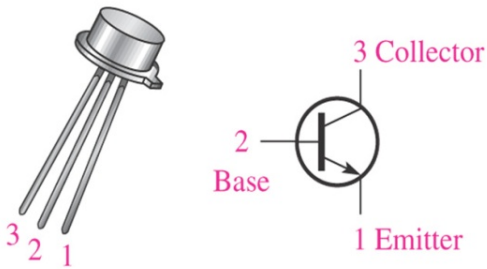

(d) TO-52 or TO-206AC




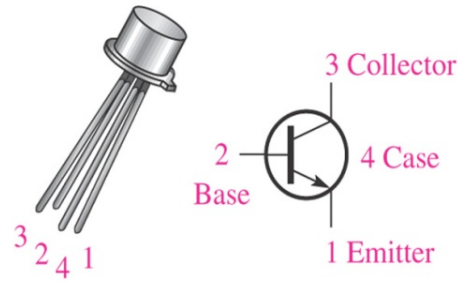


(e) TO-72 or TO-206AF

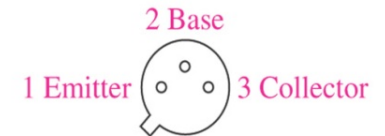

(f) Pin configuration (bottom view).  
Emitter is closest to tab.

# Power Transistors

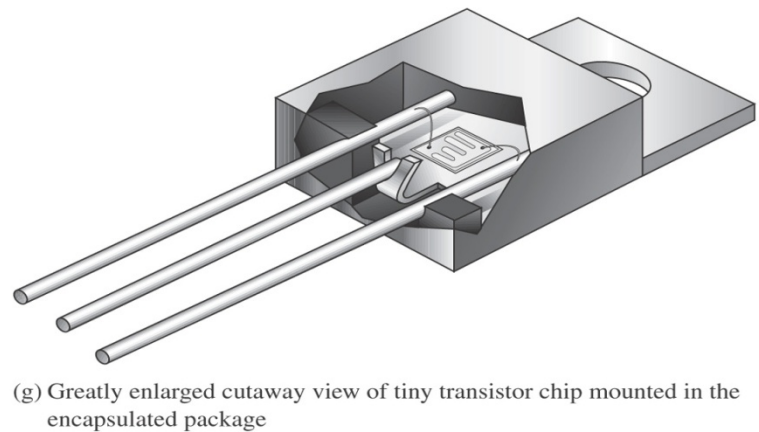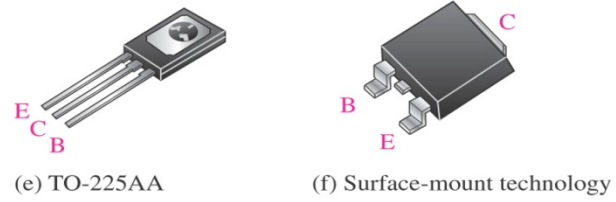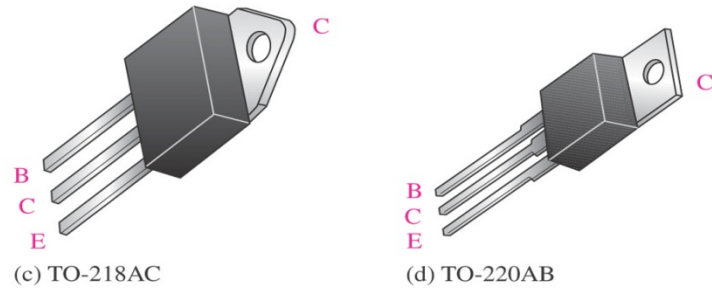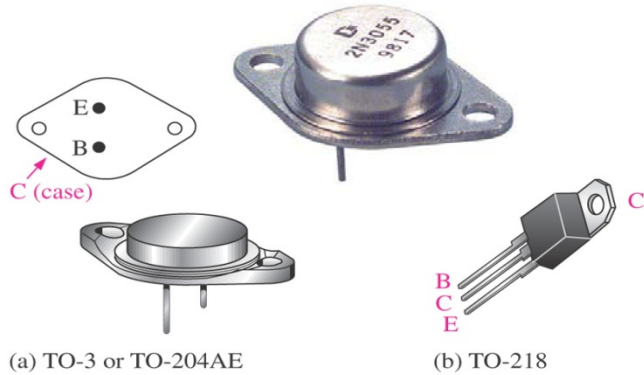

### Maximum Ratings

Rating	Symbol	Value	Unit
Collector-Emitter voltage	$V_{CEO}$	40	V dc
Collector-Base voltage	$V_{CBO}$	60	V dc
Emitter-Base voltage	$V_{EBO}$	6.0	V dc
Collector current — continuous	$I_C$	200	mA dc
Total device dissipation @ $T_A = 25^\circ\text{C}$ Derate above $25^\circ\text{C}$	$P_D$	625 5.0	mW mW/ $^\circ\text{C}$
Total device dissipation @ $T_C = 25^\circ\text{C}$ Derate above $25^\circ\text{C}$	$P_D$	1.5 12	Watts mW/ $^\circ\text{C}$
Operating and storage junction Temperature range	$T_J, T_{stg}$	-55 to +150	$^\circ\text{C}$

### Thermal Characteristics

Characteristic	Symbol	Max	Unit
Thermal resistance, junction to case	$R_{\theta JC}$	83.3	$^\circ\text{C/W}$
Thermal resistance, junction to ambient	$R_{\theta JA}$	200	$^\circ\text{C/W}$



### Electrical Characteristics ( $T_A = 25^\circ\text{C}$ unless otherwise noted.)

Characteristic	Symbol	Min	Max	Unit
<b>OFF Characteristics</b>				
Collector-Emitter breakdown voltage ( $I_C = 1.0$ mA dc, $I_B = 0$ )	$V_{(BR)CEO}$	40	—	V dc
Collector-Base breakdown voltage ( $I_C = 10$ $\mu\text{A}$ dc, $I_E = 0$ )	$V_{(BR)CBO}$	60	—	V dc
Emitter-Base breakdown voltage ( $I_E = 10$ $\mu\text{A}$ dc, $I_C = 0$ )	$V_{(BR)EBO}$	6.0	—	V dc
Base cutoff current ( $V_{CE} = 30$ V dc, $V_{EB} = 3.0$ V dc)	$I_{BL}$	—	50	nA dc
Collector cutoff current ( $V_{CE} = 30$ V dc, $V_{EB} = 3.0$ V dc)	$I_{CEX}$	—	50	nA dc

### ON Characteristics

DC current gain ( $I_C = 0.1$ mA dc, $V_{CE} = 1.0$ V dc)	2N3903 2N3904	$h_{FE}$	20 40	— —	—
( $I_C = 1.0$ mA dc, $V_{CE} = 1.0$ V dc)	2N3903 2N3904		35 70	— —	
( $I_C = 10$ mA dc, $V_{CE} = 1.0$ V dc)	2N3903 2N3904		50 100	150 300	
( $I_C = 50$ mA dc, $V_{CE} = 1.0$ V dc)	2N3903 2N3904		30 60	— —	
( $I_C = 100$ mA dc, $V_{CE} = 1.0$ V dc)	2N3903 2N3904		15 30	— —	
Collector-Emitter saturation voltage ( $I_C = 10$ mA dc, $I_B = 1.0$ mA dc) ( $I_C = 50$ mA dc, $I_B = 5.0$ mA dc)		$V_{CE(sat)}$	— —	0.2 0.3	V dc
Base-Emitter saturation voltage ( $I_C = 10$ mA dc, $I_B = 1.0$ mA dc) ( $I_C = 50$ mA dc, $I_B = 5.0$ mA dc)		$V_{BE(sat)}$	0.65 —	0.85 0.95	V dc

2N3903  
2N3904

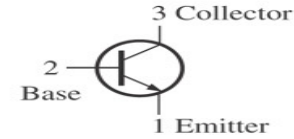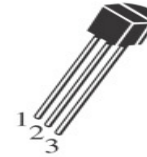


General-Purpose  
Transistors

NPN Silicon



# Example

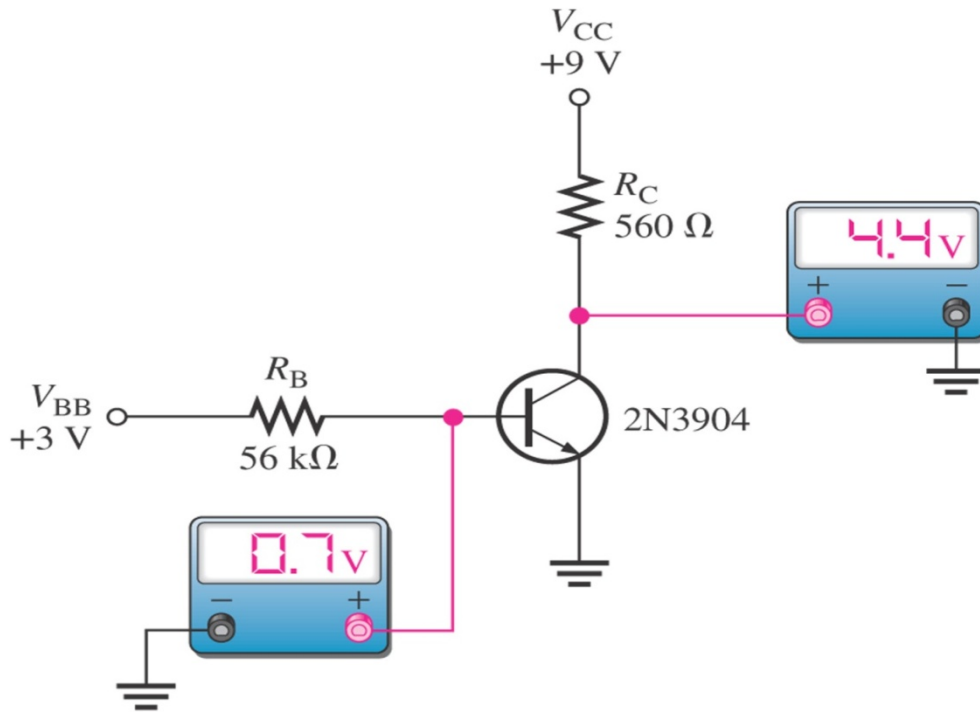


Find beta or  $h_{FE}$  or dc current gain

= \_\_\_\_\_

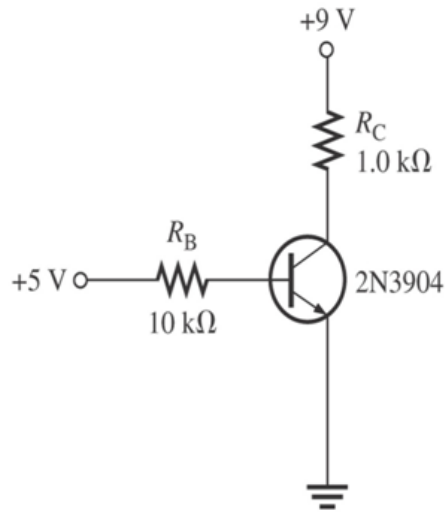
# Example



Refer to the datasheet. Determine whether or not the transistor is saturated in each circuit based on the maximum specific value of  $h_{FE}$ .



(a)

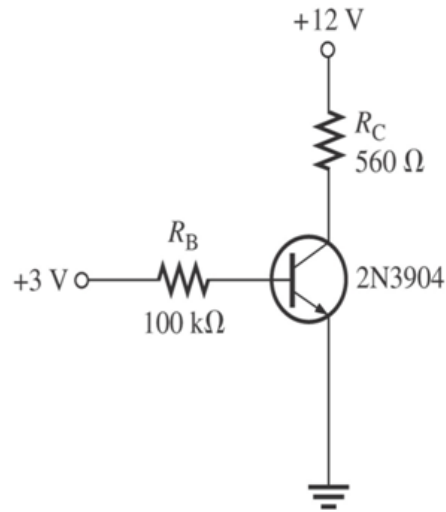

(b)

# BC547 NPN TRANSISTOR

## ELECTRICAL CHARACTERISTICS

	Symbol	Min.	Typ.	Max.	Unit
DC Current Gain at $V_{CE} = 5\text{ V}$ , $I_C = 10\mu\text{A}$					
<b>Current Gain Group A</b>	$h_{FE}$	–	90	–	–
<b>B</b>	$h_{FE}$	–	150	–	–
<b>C</b>	$h_{FE}$	–	270	–	–
at $V_{CE} = 5\text{ V}$ , $I_C = 2\text{ mA}$					
<b>Current Gain Group A</b>	$h_{FE}$	110	180	220	–
<b>B</b>	$h_{FE}$	200	290	450	–
<b>C</b>	$h_{FE}$	420	500	800	–
at $V_{CE} = 5\text{ V}$ , $I_C = 100\text{ mA}$					
<b>Current Gain Group A</b>	$h_{FE}$	–	120	–	–
<b>B</b>	$h_{FE}$	–	200	–	–
<b>C</b>	$h_{FE}$	–	400	–	–
Thermal Resistance Junction to Ambient Air	$R_{thJA}$	–	–	250 <sup>1)</sup>	K/W
Collector Saturation Voltage at $I_C = 10\text{ mA}$ , $I_B = 0.5\text{ mA}$ at $I_C = 100\text{ mA}$ , $I_B = 5\text{ mA}$	$V_{CEsat}$ $V_{CEsat}$	– –	80 200	200 600	mV mV
Base Saturation Voltage at $I_C = 10\text{ mA}$ , $I_B = 0.5\text{ mA}$ at $I_C = 100\text{ mA}$ , $I_B = 5\text{ mA}$	$V_{BEsat}$ $V_{BEsat}$	– –	700 900	– –	mV mV
Base-Emitter Voltage at $V_{CE} = 5\text{ V}$ , $I_C = 2\text{ mA}$ at $V_{CE} = 5\text{ V}$ , $I_C = 10\text{ mA}$	$V_{BE}$ $V_{BE}$	580 –	660 –	700 720	mV mV
Collector-Emitter Cutoff Current at $V_{CE} = 80\text{ V}$ at $V_{CE} = 50\text{ V}$	$I_{CES}$ $I_{CES}$	– –	0.2 0.2	15 15	nA nA
at $V_{CE} = 30\text{ V}$	$I_{CES}$	–	0.2	15	nA
at $V_{CE} = 80\text{ V}$ , $T_j = 125\text{ }^\circ\text{C}$ at $V_{CE} = 50\text{ V}$ , $T_j = 125\text{ }^\circ\text{C}$	$I_{CES}$ $I_{CES}$	– –	– –	4 4	$\mu\text{A}$ $\mu\text{A}$

# Hint for $h_{FE}$ Selection




The datasheet shows that the  $h_{FE}$  can not be specified precisely by the manufacturer, because it varies very much between transistors and with electrical and thermal conditions. However, it is possible to get an approximated value.

Students can start with the roughly calculation of  $I_C$ . For example, if  $I_C = 20\text{mA}$ , we can take an intermediate value between the  $h_{FE}$  for  $I_C = 2\text{mA}$  (500) and the  $h_{FE}$  for  $I_C = 100\text{mA}$  (400), so let's take  $h_{FE} = 450$ .
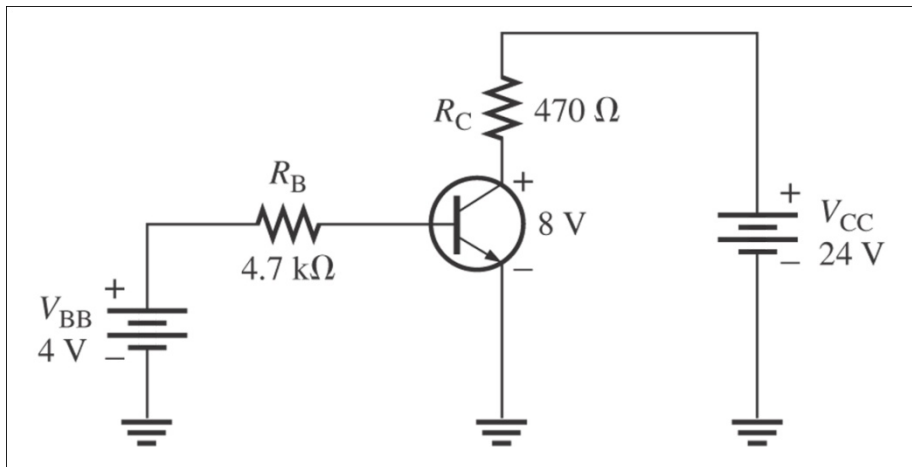
# Example




- Determine  $I_B, I_C, I_E$  and  $\beta_{DC}$ .


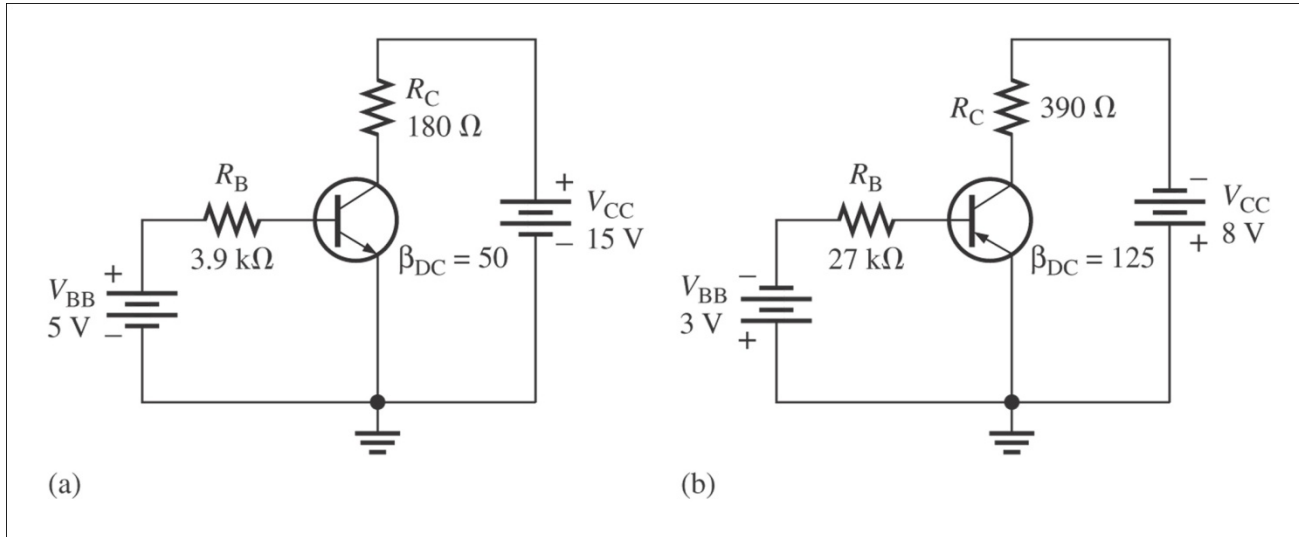
# Example




- Find  $V_{CE}$ ,  $V_{BE}$ ,  $V_{CB}$  in both circuits.


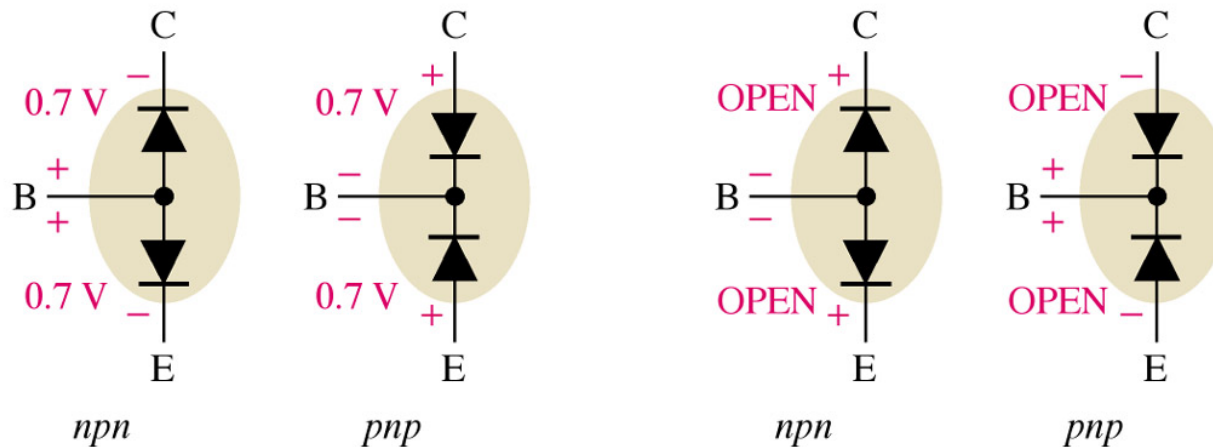
# Testing Transistors



Testing a transistor can be viewed more simply if you view it as testing two diode junctions. Forward bias having low resistance and reverse bias having infinite resistance.




(a) Both junctions should read  $0.7\text{ V} \pm 0.2\text{ V}$  when forward-biased.

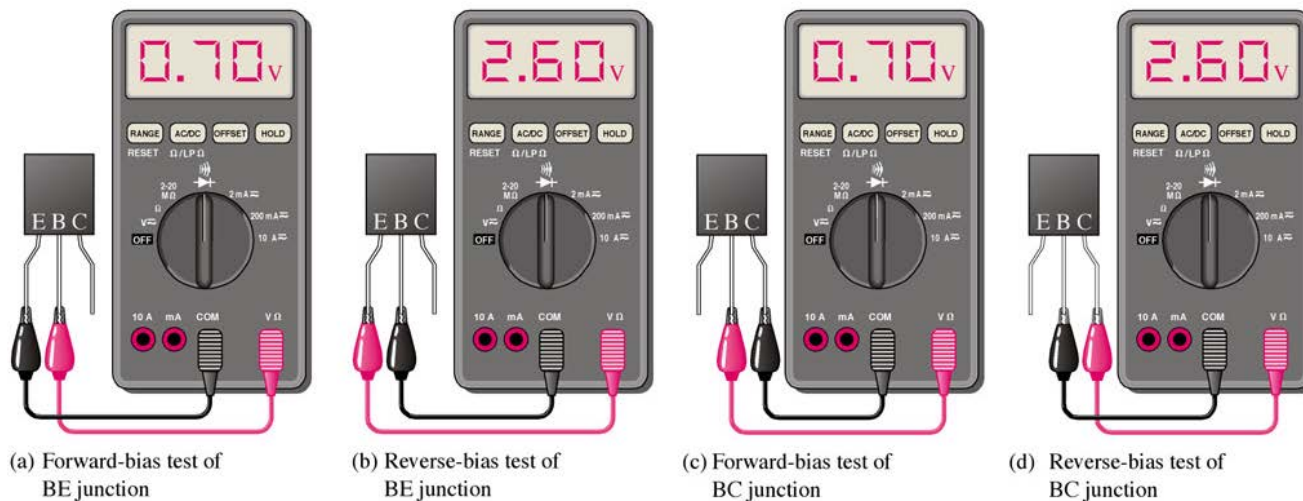(b) Both junctions should ideally read OPEN when reverse-biased.



The diode test function of a multimeter is more reliable than using an ohmmeter. Make sure to note whether it is an npn or pnp and polarize the test leads accordingly.



In addition to the traditional DMMs there are also transistor testers. Some of these have the ability to test other parameters of the transistor, such as leakage and gain. Curve tracers give us even more detailed information about a transistors characteristics.



# Conclusions



- The bipolar junction transistor (BJT) is constructed of three regions: base, collector, and emitter.
- The BJT has two pn junctions, the base-emitter junction and the base-collector junction.
- The two types of transistors are pnp and npn.
- For the BJT to operate as an amplifier, the base-emitter junction is forward-biased and the collector-base junction is reverse-biased.
- Of the three currents  $I_B$  is very small in comparison to  $I_E$  and  $I_C$ .
- Beta is the current gain of a transistor. This is the ratio of  $I_C/I_B$ .



- A transistor can be operated as an electronics switch.
- When the transistor is off it is in cutoff condition (no current).
- When the transistor is on, it is in saturation condition (maximum current).
- Beta can vary with temperature and also varies from transistor to transistor.





---

# Supplement




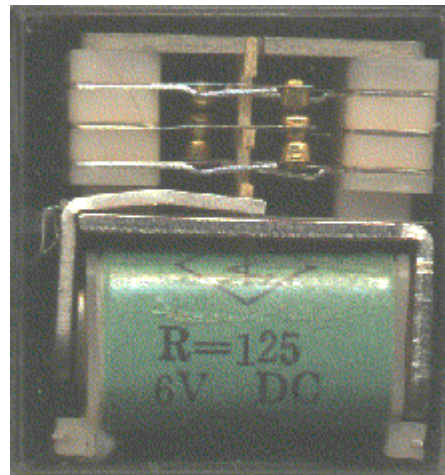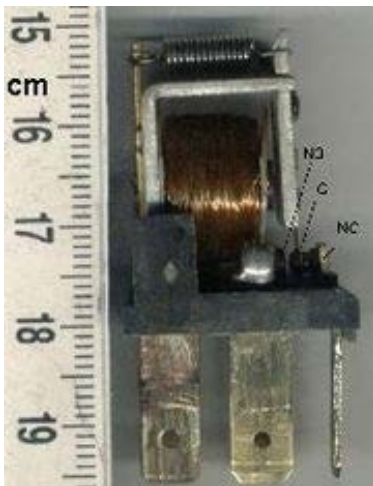
# Relays


- A relay is an **electrically operated switch**. Current flowing through the coil of the relay creates a magnetic field which attracts a lever and changes the switch contacts. The coil current can be on or off so relays have two switch positions and they are **double throw (changeover)** switches.




Symbol

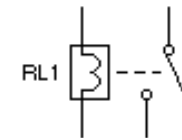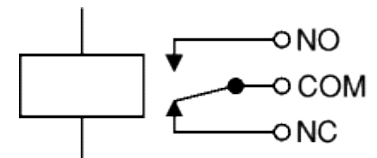



SPDT  
Relays

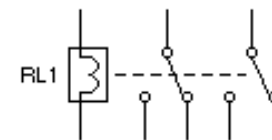

DPDT  
Relays

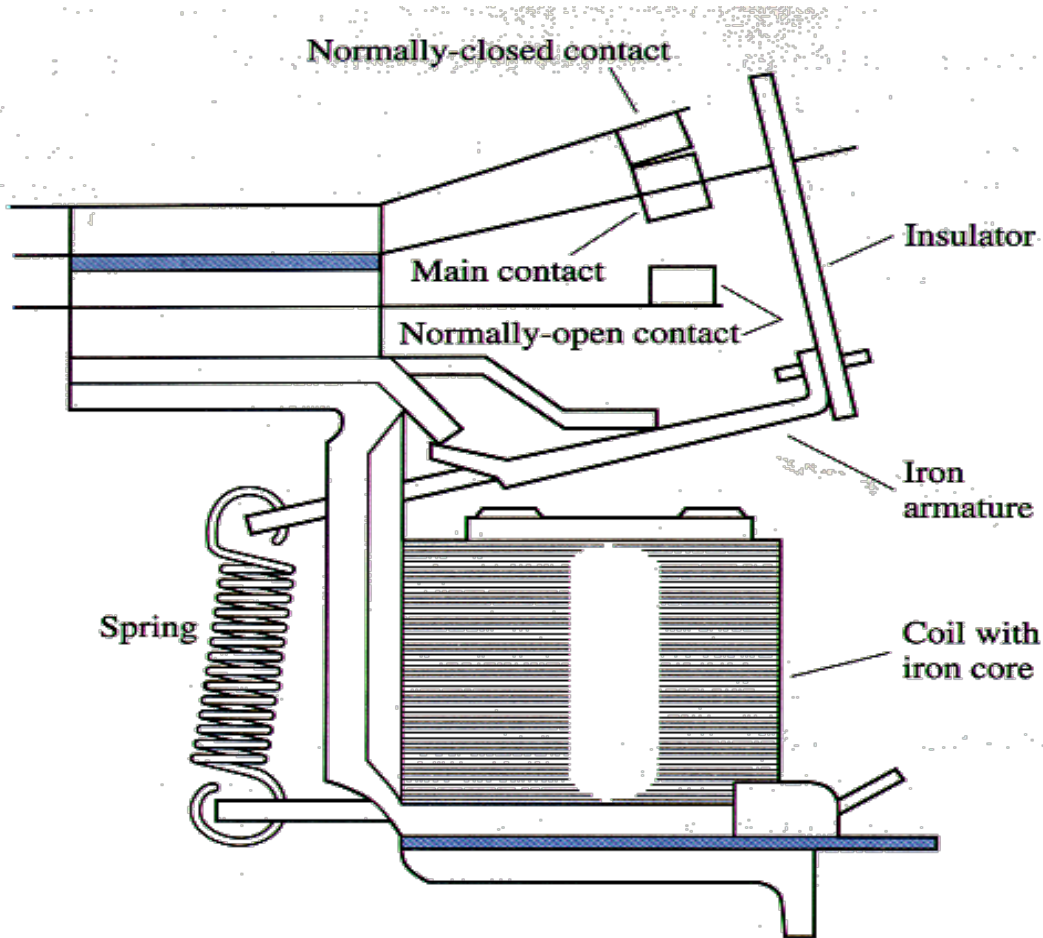

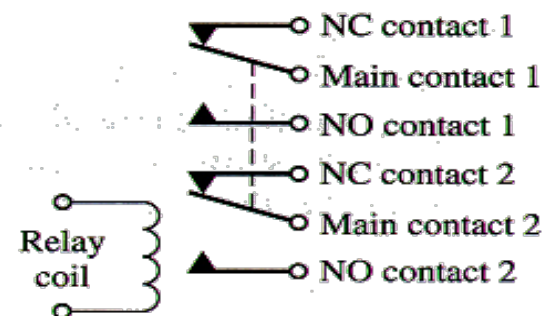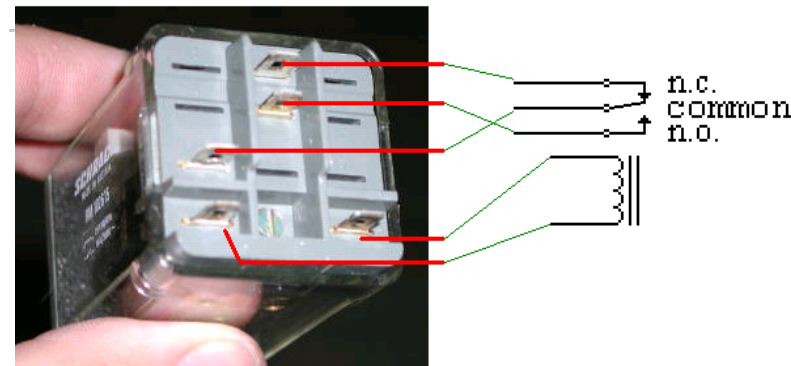(a) Physical structure of the electromechanical relay



(b) Schematic representation of a relay with DPDT contacts